

Unit - 1

Number System

→ Convert Binary to Decimal

$$\text{Q1} \quad (10101)_2 \rightarrow 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ = 16 + 0 + 4 + 0 + 1 \\ = (21)_{10}$$

→ Convert Decimal to Binary

Q1 $(21)_{10}$

$21 \div 2 \quad 1$ LSB → least significant bit

$10 \div 2 \quad 0$

$5 \div 2 \quad 1$

$2 \div 2 \quad 0$

1 MSB → Most significant bit

* Binary = 0-1

Octal = 0-7

Decimal = 0-9

Hexadecimal = 0-F

$2^2 \quad 2^1 \quad 2^0$	
$1 = 0 \quad 0 \quad 1$	$10 = A$

$2 = 0 \quad 1 \quad 0$	$11 = B$
-------------------------	----------

$3 = 0 \quad 1 \quad 1$	$12 = C$
-------------------------	----------

$4 = 1 \quad 0 \quad 0$	$13 = D$
-------------------------	----------

$5 = 1 \quad 0 \quad 1$	$14 = E$
-------------------------	----------

$6 = 1 \quad 1 \quad 0$	$15 = F$
-------------------------	----------

Shrikumar 11

→ Convert Binary into decimal

1] $(101110)_2$

$$= 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$$

$$= 32 + 0 + 8 + 4 + 2 + 0$$

$$= (46)_{10}$$

2] $(000011)_2$

$$= 0 + 0 + 0 + 2 + 1$$

$$= (3)_{10}$$

3] $(1000011)_2$

$$= 1 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

$$= 32 + 0 + 0 + 0 + 2 + 1$$

$$= (35)_{10}$$

→ Convert decimal to binary

1] $(21)_{10}$

$$21 \div 2 \quad 1$$

$$10 \div 2 \quad 0$$

$$5 \div 2 \quad 1$$

$$(10101)_2$$

$$2 \div 2 \quad 0$$

$$\vdots$$

2] $(29)_{10}$

$$29 \div 2 \quad 1$$

$$14 \div 2 \quad 0$$

$$(11101)_2$$

$$7 \div 2 \quad 1$$

$$3 \div 2 \quad 1$$

$$1 \div 2 \quad 1$$

→ Convert to Octal to decimal

$$1] (215)_8$$

$$= 2 \times 8^2 + 1 \times 8^1 + 5 \times 8^0$$

$$= 128 + 8 + 5$$

$$= (141)_{10}$$

$$2] (12570)_8$$

$$= 1 \times 8^4 + 2 \times 8^3 + 5 \times 8^2 + 7 \times 8^1 + 0 \times 8^0$$

$$= 4096 + 1024 + 320 + 56 + 0$$

$$= (5496)_{10}$$

$$3] (5496)_8$$

$$= 5 \times 8^3 + 4 \times 8^2 + 9 \times 8^1 + 6 \times 8^0$$

$$= 2560 + 256 + 72 + 6$$

$$= (4894)_{10}$$

→ Convert binary to Octal

$$1] (\underline{10101})_2$$

$$(25)_8$$

$$2] (\underline{1100111})_2$$

$$(147)_8$$

$$3] (\underline{101011})_2$$

$$(53)_8$$

→ Octal to Binary

i] $(25)_8$

$$\begin{array}{r} 2 \quad 5 \\ 010 \quad 101 \\ = (10101)_2 \end{array}$$

ii] $(29)_8$

$\begin{array}{r} 2 \quad 9 \\ \times \quad \text{Not possible} \end{array}$

iii] $(346)_8$

$$\begin{array}{r} 3 \quad 4 \quad 6 \\ 011 \quad 100 \quad 110 \\ = (011100110)_2 \end{array}$$

→ Convert binary to Hexadecimal

i] $(10101)_2$

= $(15)_H$

= $(F)_H$

→ Convert Hexadecimal to binary

i] $(12EA)_{16}$

$$\begin{array}{cccc} 0001 & 0010 & 1110 & 1010 \\ | & 2 & E & A \end{array}$$

$(000100101101010)_2$

→ Convert binary to Decimal, Octal and Hexadecimal

$$1] (1011011)_2 = (?)_{10} \quad (?)_8 \quad (?)_{16}$$

$$(?)_{10}$$

$$= 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

$$= 64 + 0 + 16 + 8 + 0 + 0 + 1 = 81$$

$$= (91)_{10}$$

$$(?)_8$$

$$(1011011)$$

$$= (133)_8$$

$$(?)_{16}$$

$$(1011011)$$

$$= (5B)_{16}$$

$$2] (1001001)_2 = (?)_{10} \quad (?)_8 \quad (?)_{16}$$

$$(?)_{10}$$

$$= 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

$$= 64 + 0 + 0 + 8 + 0 + 0 + 1$$

$$= (75)_{10}$$

$$(?)_8$$

$$(1001001)$$

$$= (111)_8$$

$$(?)_{16}$$

$$(1001001)$$

$$(49)_{16}$$

3] $(100001)_2 = (?)_{10} (?)_8 (?)_{16}$
 $= 1 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$
 $= 32 + 0 + 0 + 0 + 0 + 1$
 $= (33)_{10}$
 $= (41)_8$
 $= (21)_{16}$

4] $(10011101)_2 = (?)_{10} (?)_8 (?)_{16}$
 $= 1 \times 2^7 + 0 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$
 $= 128 + 0 + 0 + 16 + 8 + 4 + 0 + 1$
 $= (157)_{10}$
 $= (235)_8$
 $= (9D)_{16}$

5] $(1011010)_2 = (?)_{10}$
 $= 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$
 $= 64 + 0 + 16 + 8 + 0 + 2 + 0$
 $= (90)_{10}$

6] $(011001.1011)_2 = (?)_8 (?)_{16}$
 $= (31.54)_8$
 $= (19.B)_{16}$

→ Conversion

$$1] (101011)_2 = (?)_{10}$$

$$= 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

$$= 32 + 0 + 8 + 0 + 2 + 1$$

$$= (43)_{10}$$

$$2] (1101)_2 = (?)_{10}$$

$$= 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

$$= 8 + 4 + 0 + 1$$

$$= (13)_{10}$$

$$3] (111001)_2 = (?)_8$$

$$= \underline{\underline{1}} \underline{\underline{1}} \underline{\underline{1}} \underline{\underline{0}} \underline{\underline{0}} \underline{\underline{1}}$$

$$= \underline{1} \quad \underline{1}$$

$$= (71)_8$$

$$4] (1100011)_2 = (?)_8$$

$$= \underline{\underline{1}} \underline{\underline{1}} \underline{\underline{0}} \underline{\underline{0}} \underline{\underline{0}} \underline{\underline{1}} \underline{\underline{1}}$$

$$= \underline{1} \quad \underline{4} \quad \underline{3}$$

$$= (143)_8$$

$$5] (111001.1011)_2 = (?)_8$$

$$= (71, 54)_8$$

$$6] (1110011)_2 = (163) (?)_{16}$$

$$= (73)_{16}$$

$$7] (1100011.01)_2 = (?)_{16} = (18D)_{16}$$

→ Convert decimal to binary

1) $(13)_{10} = (?)_2$

	Quotient	Remainder	
$13 \div 2$	6	1	LSB
$6 \div 2$	3	0	
$3 \div 2$	1	1	
$1 \div 2$	0	1	MSB ↑

$$(13)_{10} = (1101)_2$$

2) $(174)_{10} = (?)_2$

$174 \div 2$	87	0
$87 \div 2$	43	1
$43 \div 2$	21	1
$21 \div 2$	10	1
$10 \div 2$	5	0
$5 \div 2$	2	1
$2 \div 2$	1	0
		1

$$= (10101110)_2$$

→ Convert Decimal to Hexadecimal Octal
 3] $(501)_{10} = (?)_8$

	Quotient	Remainder
$501 \div 8$	62.625	$0.625 \times 8 = 5$
$62 \div 8$	7.75	$0.75 \times 8 = 6$
$7 \div 8$	0.875	$0.875 \times 8 = 7$

$$(501)_{10} = (765)_8$$

4] $(1465)_{10} = (?)_8$

$1465 \div 8$	183.125	$0.125 \times 8 = 1$
$183 \div 8$	22.875	$0.875 \times 8 = 7$
$22 \div 8$	2.75	$0.75 \times 8 = 6$
$2 \div 8$	0.25	$0.25 \times 8 = 2$

$$(1465)_{10} = (2671)_8$$

→ Convert Decimal to Hexadecimal

$(501)_{10} = (?)_{16}$

	Quotient	Remainder
$501 \div 16$	31.3125	$0.3125 \times 16 = 5$
$31 \div 16$	1.9375	$0.9375 \times 16 = 15 = F$
$1 \div 16$	0.0625	$0.0625 \times 16 = 1$

$$(1F5)_{16}$$

→ Decimal to Binary

$$(501)_{10} = (?)_2$$

	Quotient	Remainder
$501 \div 2$	250	1
$250 \div 2$	125	0
$125 \div 2$	62	1
$62 \div 2$	31	0
$31 \div 2$	15	1
$15 \div 2$	7	1
$7 \div 2$	3	1
$3 \div 2$	1	1
$1 \div 2$	0	1

→ Octal to Binary

$$\bullet \quad (205)_3 = (?)_2$$

11 00 1015

= 010 000 101

$$= (010000101),$$

$$\rightarrow (205)_8 = (?)_{10} \rightarrow (?)_2$$

$$= 2 \times 8^2 + 0 \times 8^1 + 5 \times 8^0$$

$$= 128 + 0 + 5$$

$$= (133)_{10} \rightarrow (?)_7$$

$$= (10001101)_2$$

$$(+33)_{10} = (001011011)_2$$

$$133 \div 2 = 66$$

$$66 \div 2 = 33$$

$$33 \div 2$$

$$16 \div ?$$

$$8 \div 2 = 0$$

$$4 \div 2 = 0$$

$$2 \div 2 = 0$$

→ Decimal to Hexadecimal

1] $(4253)_{10} = (?)_H$

$4253 \div 16$	265.8125	$8125 \times 16 = D$
$265 \div 16$	16.5625	$5625 \times 16 = 9$
$16 \div 16$	1	$0 \times 16 = 0$
$1 \div 16$	0.0625	$0625 \times 16 = 1$

$$(4253)_{10} = (109D)_{16}$$

2] $(252)_{10} = (?)_H$

$252 \div 16$	15.75	C
$15 \div 16$	0.9375	F

$$(252)_{10} = (CF)_{10} (FC)_{16}$$

3] $(289)_{10} = (?)_H$

$289 \div 16$	18.0625	I
$18 \div 16$	1.125	2
$1 \div 16$	0.0625	I

$$(289)_{10} = (121)_{16}$$

4] $(3333)_{10} = (?)_H$

$3333 \div 16$	208.3125	5
$208 \div 16$	13	0
$13 \div 16$	0.8125	D

$$(3333)_{10} = (D05)_{16}$$

5] $(5749)_{10} = (?)_H = (1675)_H$

$5749 \div 16$	359.3125	5	$92 \div 16$	1.375	6
359.3125	22.4375	7	$1 \div 16$	0.0625	1

→ Convert Hexadecimal to decimal

$$\begin{aligned} 1] \quad (A210)_H &= (?)_{10} \\ &= 10 \times 16^3 + 2 \times 16^2 + 1 \times 16^1 + 0 \times 16^0 \\ &= 40960 + 512 + 16 + 0 \\ &= (41488)_{10} \end{aligned}$$

$$\begin{aligned} 2] \quad (459)_H &= (?)_{10} \\ &= 4 \times 16^2 + 5 \times 16^1 + 9 \times 16^0 \\ &= 1024 + 80 + 9 \\ &= 1113 \end{aligned}$$

$$\begin{aligned} 3] \quad (92F)_H &= (?)_{10} \\ &= 9 \times 16^2 + 2 \times 16^1 + 15 \times 16^0 \\ &= 2304 + 32 + 15 \\ &= 2351 \end{aligned}$$

→ Convert Hexadecimal to octal

$$1] \quad (981)_H \rightarrow (?)_8$$

1st convert $(981)_H \rightarrow (?)_2$ and then into octal

$$(981)_H = (100110000001)_2$$

$$\begin{aligned} (100110000001)_2 &= (?)_8 \\ &= (4601)_8 \end{aligned}$$

$$2] \quad (FF)_H = (?)_8$$

$$(FF)_H = (?)_2 = (11111111)_2$$

$$\begin{aligned} (11111111)_2 &= (?)_8 \\ &= (317)_8 \end{aligned}$$

→ Octal to Decimal

$$\begin{aligned} 1] \quad (756)_8 &= (?)_{10} \\ &= 7 \times 8^2 + 5 \times 8^1 + 6 \times 8^0 \\ &= 448 + 40 + 6 \\ &= (496)_{10} \end{aligned}$$

$$\begin{aligned} 2] \quad (1034)_8 &= (?)_{10} \\ &= 1 \times 8^3 + 0 \times 8^2 + 3 \times 8^1 + 4 \times 8^0 \\ &= 512 + 0 + 24 + 4 \\ &= (540)_{10} \end{aligned}$$

$$\begin{aligned} 3] \quad (5602)_8 &= (?)_{10} \\ &= 5 \times 8^3 + 6 \times 8^2 + 0 \times 8^1 + 2 \times 8^0 \\ &= 2560 + 384 + 0 + 2 \\ &= (2946)_{10} \end{aligned}$$

→ Hexadecimal to binary

$$\begin{aligned} 1] \quad (A2B)_{16} &= (?)_2 \\ (A2B)_{16} &= (?)_{10} \\ &= A \times 16^2 + 2 \times 16^1 + B \times 16^0 \\ &= 2560 + 32 + 11 \\ &= (2603)_{10} \end{aligned}$$

$$\begin{array}{rcl} (2603)_{10} & = & 2603 \div 2 & | \\ & & 1301 \div 2 & | \\ & & 650 \div 2 & | \\ & & 325 \div 2 & | \\ & & 162 \div 2 & | \end{array}$$

$$\begin{array}{r}
 81 \div 2 & 1 \\
 40 \div 2 & 0 \\
 20 \div 2 & 0 \\
 10 \div 2 & 0 \\
 5 \div 2 & 0 \\
 2 \div 2 & 0 \\
 & 1
 \end{array}$$

$$(2603)_{10} = (101000101011)_2$$

→ Convert octal into decimal and then into binary

$$\begin{aligned}
 17 \quad (540)_{10} &= (?)_{10} \rightarrow (?)_2 \\
 &= 5 \times 8^2 + 4 \times 8^1 + 0 \times 8^0 \\
 &= 320 + 32 + 0 \\
 &= (352)_{10}
 \end{aligned}$$

$$\begin{array}{r}
 352 \div 2 & 0 \\
 176 \div 2 & 0 \\
 88 \div 2 & 0 \\
 44 \div 2 & 0 \\
 22 \div 2 & 0 \\
 11 \div 2 & 1 \\
 5 \div 2 & 1 \\
 2 \div 2 & 0 \\
 & 1
 \end{array}$$

$$(352)_{10} = (101100000)_2$$

2] $(667)_8 = (?)_{10} \rightarrow (?)_2$

$$\begin{aligned}
 &= 6 \times 8^2 + 6 \times 8^1 + 7 \times 8^0 \\
 &= 384 + 48 + 7 \\
 &= (439)_{10}
 \end{aligned}$$

$$\begin{array}{r}
 439 \div 2 \quad | \\
 219 \div 2 \quad | \\
 109 \div 2 \quad | \\
 54 \div 2 \quad 0 \\
 27 \div 2 \quad | \\
 13 \div 2 \quad | \\
 6 \div 2 \quad 0 \\
 3 \div 2 \quad | \\
 1 \div 2 \quad |
 \end{array}$$

$$(439)_{10} = (110110111)_2$$

3] $(352)_8 = (?)_{10} \rightarrow (?)_8$

$$\begin{aligned}
 &= 3 \times 8^2 + 5 \times 8^1 + 2 \times 8^0 \\
 &= 192 + 40 + 2 \\
 &= (234)_{10}
 \end{aligned}$$

$$\begin{array}{r}
 234 \div 2 \quad 0 \\
 117 \div 2 \quad 1 \\
 58 \div 2 \quad 0 \\
 29 \div 2 \quad 1 \\
 14 \div 2 \quad 0 \\
 7 \div 2 \quad 1 \\
 3 \div 2 \quad 1 \\
 1 \div 2 \quad 1
 \end{array}$$

$$(234)_{10} = (11101010)_2$$

4] $(157)_8 = (?)_{10} \rightarrow (?)_2$

$$\begin{aligned}
 &= 1 \times 8^3 + 5 \times 8^2 + 7 \times 8^0 \\
 &= 64 + 40 + 7 \\
 &= (111)_10
 \end{aligned}$$

$$\begin{array}{r|l}
 111 & 2 \\
 55 & 2 \\
 27 & 2 \\
 13 & 2 \\
 6 & 2 \\
 3 & 2 \\
 1 & 2
 \end{array}$$

$$(111)_{10} = (110111)_2$$

5) $(6273)_8 = (?)_{10} \rightarrow (?)_2$

$$\begin{aligned}
 &= 6 \times 8^3 + 2 \times 8^2 + 7 \times 8^1 + 3 \times 8^0 \\
 &= 3072 + 128 + 56 + 3 \\
 &= (3259)_{10}
 \end{aligned}$$

$$\begin{array}{r|l}
 3259 & 2 \\
 1629 & 2 \\
 814 & 2 \\
 402 & 2 \\
 201 & 2 \\
 100 & 2 \\
 50 & 2 \\
 25 & 2 \\
 12 & 2 \\
 6 & 2 \\
 3 & 2
 \end{array}$$

$$(3259)_{10} = (110010010011)_2$$

1] $(1101.011)_2 = (?)_{10}$

$$= 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 0 \times 2^{-1} + 1 \times 2^{-2} + 1 \times 2^{-3}$$

$$= 8 + 4 + 0 + 1 + 0 + \frac{1}{4} + \frac{1}{8}$$

$$= (13.375)_{10}$$

2] $(276.43)_8 = (?)_{10}$

$$= 2 \times 64 + 7 \times 8 + 6 \times 8^0 + 4 \times 8^{-1} + 3 \times 8^{-2}$$

$$= 128 + 56 + 6 + \frac{4}{8} + \frac{3}{64}$$

$$= (190.546875)_{10}$$

3] $(A1.23)_{16} = (?)_{10}$

$$= 10 \times 16 + 1 \times 16^0 + 2 \times 16^{-1} + 3 \times 16^{-2}$$

$$= 160 + 1 + \frac{1}{8} + \frac{3}{256}$$

$$= (161.136)_{10}$$

4] $(88.37)_{10} = (?)_8$

$(88)_{10} = (?)_8$

$$\begin{array}{r} 88 \div 8 = 11 \\ 11 \div 8 = 1.375 \\ 1.375 \div 8 = 0.125 \end{array}$$

$(88.37)_{10} = (130)_8$

$(.37)_8 = (?)_{10}$

$0.37 \times 8 = 2.96 \quad 2$

$0.96 \times 8 = 7.68 \quad 7$

$0.68 \times 8 = 5.44 \quad 5$

$0.44 \times 8 = 3.52 \quad 3$

$0.52 \times 8 = 4.16 \quad 4$

$(0.37)_8 = \cancel{(43572)}_{(255 \cdot 21534)}$

$(88.37)_{10} = (130.27534)_8$

$$(27.47)_{10} = (?)_8$$

$$\begin{array}{r} 2 \times 8^2 + 7 \times 8^1 + 4 \times 8^0 + 7 \times 8^{-1} \\ = 16 + 7 + 1/2 + 7/8 \\ = 24.875 \end{array}$$

F 22.

$$5) (27.47)_{10} = (?)_8$$

$$(27)_{10} = (?)_8$$

$$27 \div 8 \quad 3.375$$

$$3 \div 8 \quad 0.375$$

$$(27)_{10} = (33)_8$$

$$(0.47)_{10} = (?)_8$$

$$0.47 \times 8 = 3.76 \quad 3$$

$$0.76 \times 8 = 6.08 \quad 6$$

$$0.08 \times 8 = 0.64 \quad 0$$

$$0.64 \times 8 = 5.12 \quad 5$$

$$0.12 \times 8 = 0.96 \quad 0$$

$$(0.47)_{10} = (3605)_8$$

$$(27.47)_{10} = (33.3605)_8$$

$$6) (27.47)_{10} = (?)_{16}$$

$$(27)_{10} = (?)_{16}$$

$$27 \div 16 = 1.6875$$

$$= 27 \div 16 \quad 1.6875 \quad 11 = B$$

$$1 \div 16 \quad 0.0625$$

$$(27)_{10} = (1B)_{16}$$

$$(0.47)_{10} = (?)_{16}$$

$$0.47 \times 16 = 7.52 \quad 7$$

$$0.52 \times 16 = 8.32 \quad 8$$

$$0.32 \times 16 = 5.12 \quad 5$$

$$0.12 \times 16 = 1.92 \quad 1$$

$$(0.47)_{10} = (1851)_{16}$$

$$(27.47)_{10} = (1B.7851)_{16}$$

BCD (Binary coded decimal)

0	00	0000	
1	01	0001	
2	10	0010	8421
3	11	0011	2421 } 5211 } Weighted code
4	100	0100	
5	101	0101	
6	110	0110	excess-3 ? Non
7	111	0111	gray code } weighted code
8	1000	1000	
9	1001	1001	

1] $(15)_{10} = (?)_{\text{excess-3}}$

$$\begin{array}{r}
 15 \\
 +3 +3 \\
 \hline
 48
 \end{array}
 \quad (15)_{10} = (01001000)$$

01001000

2] $(237.75)_{10} = (?)_{\text{excess-3}}$

$$\begin{array}{r}
 2 3 7.75 \\
 +3 +3 +3 +3 +3 \\
 \hline
 5 6 10 . 100 8
 \end{array}$$

$$(237.75)_{10} = (010101101010.10101000)_{\text{excess-3}}$$

→ Excess-3 to Decimal

$$1] (010101101010.10101000)_{\text{excess-3}} = (?)_{10} = (237.75)_{10}$$

010101101010.10101000

5 6 A · A 8

56A · A 8

-3-3-3-3-3

237.75

$$2] (110010100011.01110101)_{10} = (?)_{\text{excess-3}10}$$

$$\begin{array}{r} 1100 \quad 1010 \quad 0011 \quad . \quad 0111 \quad 0101 \\ -0011 \quad -0011 \quad -0011 \quad . \quad -0011 \quad -0011 \\ \hline 1001 \quad 0111 \quad 0000 \quad . \quad 0100 \quad 0010 \\ 9 \quad 7 \quad 0 \quad . \quad 4 \quad 2 \end{array}$$

$$(110010100011.01110101)_{10} = (970.42)_{\text{excess-3}10}$$

$$3] (101111100101.10001011)_{\text{excess-3}} = (?)_{10}$$

$$\begin{array}{r} 1011 \quad 1111 \quad 00101 \quad . \quad 1000 \quad 1011 \\ -0011 \quad -0011 \quad -0011 \quad . \quad -0011 \quad -0011 \\ \hline 1000 \quad 1100 \quad 0000 \quad . \quad 0101 \quad 1000 \\ 8 \quad C \quad 0 \quad . \quad 5 \quad 8 \end{array}$$

$$(1011111011.10001011)_{\text{excess-3}} = (800.58)_{10}$$

→ Decimal to Excess-3

i) $(742.48)_{10} = (?)_{\text{excess-3}}$

$$\begin{array}{r}
 7 \ 4 \ 2 \ . \ 4 \ 8 \\
 + 3 \ + 3 \ + 3 \quad + 3 \ + 3 \\
 \hline
 A \ 7 \ 5 \ . \ 7 \ B
 \end{array}$$

$$A75.7B = 101001110101.01111011$$

$$(742.48)_{10} = (101001110101.01111011)_{\text{excess-3}}$$

→ Decimal	BCD	$\times_5 - 3$	gray code
0	0000	0011	0000
1	0001	0100	0001
2	0010	0101	0011
3	0011	0110	0010
4	0100	0111	0110
5	0101	1000	0111
6	0110	1001	0101
7	0111	1010	0100
8	1000	1011	1100
9	1001	1100	1101

Sum Gray

$$0+0 = 0 \quad 0$$

$$0+1 = 1 \quad 0$$

$$1+0 = 1 \quad 0$$

$$1+1 = 0 \quad 1$$

$$(24)_{10} \longrightarrow (?)_{xs-3}$$

0010	0100
0011	0011
0101	0111

$$(24)_{10} = (01010111)_{xs-3}$$

→ Gray code

1] $(110111)_2 = (?)_{\text{gray code}}$

$\begin{array}{r} 110111 \\ \downarrow \\ (1001010)_{\text{gray code}} \end{array}$

2] $(100110)_{\text{gray code}} = (?)_2$

$\begin{array}{r} 100110 \\ \downarrow \oplus \downarrow \oplus \downarrow + \downarrow \oplus \downarrow \\ (111011)_2 \end{array}$

3] $(11011101)_2 = (?)_{\text{gray code}}$

$\begin{array}{r} 11011101 \\ \downarrow \\ (10110011)_{\text{gray code}} \end{array}$

4] $(10001001)_2$ gray code = (?)₂

10001001

↓

$(11110001)_2$

Conversion

7] $(110101)_2 = (?)_{10}$

$$= 2^5 \times 1 + 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

$$= 32 + 16 + 0 + 4 + 0 + 1$$

$$= (53)_{10}$$

2] $(101101.10101)_2 = (?)_{10}$

$$= 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 0 \times 2^{-4} +$$

$$= 32 + 0 + 8 + 4 + 0 + 1 + 1/2 + 0.5 + 0.25 + 0.125 + 0 + 0.03125$$

$$= (45.9375)_{10}$$

3] $(1111111)_2 = (?)_{10}$

$$= 1 \times 2^7 + 1 \times 2^6 + 1 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

$$= 128 + 64 + 32 + 16 + 8 + 4 + 2 + 1$$

$$= (255)_{10}$$

4] $(00000000)_2 = (?)_{10}$

$$= 0 \times 2^7 + 0 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 0 \times 2^0$$

$$= 0$$

Q

5] $(25.5)_{10} = (?)_2$

$$\begin{array}{r} 25 \div 2 \\ 12 \div 2 \\ 6 \div 2 \\ 3 \div 2 \\ 1 \div 2 \end{array} \quad \begin{array}{l} 1 \\ 0 \\ 0 \\ 1 \\ 1 \end{array}$$

$$(25)_{10} = (11101)_2$$

6] $(10.625)_{10} = (?)_2$

$$\begin{array}{r} 10 \div 2 \\ 5 \div 2 \\ 2 \div 2 \\ 1 \div 2 \end{array} \quad \begin{array}{l} 0 \\ 1 \\ 0 \\ 1 \end{array}$$

$$\begin{array}{l} 0.625 \times 2 = 1.250 \\ 0.250 \times 2 = 0.500 \\ 0.500 \times 2 = 1.000 \end{array}$$

$$(10)_{10} = (1010)_2$$

$$(10.625)_{10} = (1010.101)_2$$

7] $(0.65625)_{10} = (?)_2$

$$\begin{array}{l} 0.65625 \times 2 = 1.3125 \\ 0.3125 \times 2 = 0.625 \\ 0.625 \times 2 = 1.25 \\ 0.25 \times 2 = 0.5 \\ 0.5 \times 2 = 1 \end{array} \quad \begin{array}{l} 1 \\ 0 \\ 1 \\ 0 \\ 1 \end{array}$$

$$(0.65625)_{10} = (0.10101)_2$$

$$8] (6327.4051)_8 = (?)_{10}$$

$$= 6 \times 8^3 + 3 \times 8^2 + 2 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1} + 0 \times 8^{-2} + 5 \times 8^{-3} + 1 \times 8^{-4}$$

$$= 3072 + 192 + 16 + 7 + 0.5 + 0 + 0.00976 + 0.00024$$

$$= (3287.510004)_{10}$$

$$9] (247)_{10} = (?)_8$$

$$247 \div 8$$

$$30.875$$

$$0.875 \times 8$$

$$7$$

$$30 \div 8$$

$$3.75$$

$$0.75 \times 8$$

$$6$$

$$3 \div 8$$

$$0.375$$

$$0.375 \times 8$$

$$3$$

$$(247)_{10} = (361)_8$$

$$10] (0.6075)_{10} = (?)_8$$

$$0.6075 \times 8 = 4.86 \quad 4$$

$$0.86 \times 8 = 6.88 \quad 6$$

$$0.88 \times 8 = 7.04 \quad 7$$

$$0.04 \times 8 = 0.32 \quad 0$$

$$0.32 \times 8 = 2.56 \quad 2$$

$$0.120164 \quad (0.6075)_{10} = (0.46702)_8$$

$$11] (95.5)_{10} = (?)_{16}$$

$$95 \div 16 \quad 5.9375 \quad 15 = F$$

$$0.5 \times 16 = 8$$

$$5 \div 16 \quad 0.3125 \quad 5$$

$$(95)_{10} = (5F)_{16} \quad (0.5)_{10} = (8)_{16}$$

$$(95.5)_{10} = (5F.8)_{16}$$

12] $(675.625)_{10} = (?)_{16}$

$$\begin{array}{r} 675 \div 16 \\ 675 - 42 \cdot 1875 \\ 42 \div 16 \\ 42 - 2 \cdot 62.5 \\ 2 \div 16 \\ 2 - 0.125 \\ 0.125 \times 16 = 2 \\ 2 - 1 \\ 1 - 0 \\ 0 \end{array} \quad \begin{array}{l} 0.625 \times 16 = 10 \\ 10 = A \end{array}$$

$$(675)_{10} = (2A3)_{16}$$

$$(675.625)_{10} = (675 \cdot (2A3 \cdot A))_{16}$$

13] $(2F9A)_{16} = (?)_2$

$$\begin{array}{r} 2 F 9 A \\ 0010 1111 1001 1010 \end{array}$$

$$(2F9A)_{16} = (001011110011010)_2$$

14] Represent the decimal no. a) 27 b) 396 c) 4096
in binary form using.

- | | |
|----------------|---------------------|
| 1] Binary code | 4] Gray code |
| 2] BCD code | 5] Octal code |
| 3] XS-3 code | 6] Hexadecimal code |

→ Signed number

0 + ve
1 - ve

$$\begin{array}{l} \text{101100} \\ \text{-12} \\ \hline = 0x2^4 + 1x2^3 + 1x2^2 + 0x2^1 + 0x2^0 \\ = 0 + 8 + 4 + 0 + 0 = 12 \end{array}$$

$$\begin{array}{l} \text{01110001} \\ \text{= (+13)} \\ \hline = \cancel{0}x2^6 + 1x2^5 + 1x2^4 + 1x2^3 + 0x2^2 + 0x2^1 + 1x2^0 \\ = \cancel{0} + 64 + 32 + 16 + 0 + 0 + 1 \\ = (+13) \end{array}$$

→ Complement's code

1's
2's } Complement
9's }

$$\begin{array}{l} 1] +7 \rightarrow 0111 \rightarrow (1000)_2 \\ -7 \rightarrow 1111 \rightarrow (0000)_2 \end{array}$$

$$\begin{array}{l} +15 \rightarrow 01111 \rightarrow (10000)_2 \\ -15 \rightarrow 11111 \rightarrow (00000)_2 \end{array}$$

→ 2's compliment

$$7] (01001110)_2$$

1st convert it into 1's compliment,
then add 1 from LSB.

$$\begin{array}{r} 10110001 \\ + \\ \hline 10110000 \end{array}$$

$$\begin{array}{r} 10110001 \\ + \\ \hline 10110010 \end{array}$$

→ Arithmetic operation 2 beats

$$0+0 = \begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 0 \end{matrix}$$

$$0+1 = \begin{matrix} \text{sum} \\ 1 \end{matrix} \quad \begin{matrix} \text{carry} \\ 0 \end{matrix}$$

$$1+0 = \begin{matrix} \text{sum} \\ 1 \end{matrix} \quad \begin{matrix} \text{carry} \\ 0 \end{matrix}$$

$$1+1 = \begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

→ Arithmetic operation 3 beat

$$\begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

$$0+0+1 = \begin{matrix} \text{sum} \\ 1 \end{matrix}$$

$$0\ 1\ 0 = \begin{matrix} \text{sum} \\ 1 \end{matrix}$$

$$0\ 1\ 1 = \begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

$$1\ 0\ 0 = \begin{matrix} \text{sum} \\ 1 \end{matrix}$$

$$1\ 0\ 1 = \begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

$$1\ 1\ 0 = \begin{matrix} \text{sum} \\ 0 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

$$1\ 1\ 1 = \begin{matrix} \text{sum} \\ 1 \end{matrix} \quad \begin{matrix} \text{carry} \\ 1 \end{matrix}$$

→ 9's compliment

$$\text{if } (29)_{10} = (?)_9$$

$$9\ 9$$

$$- 2\ 9$$

$$(29)_{10} = (70)_9 \text{ 9's}$$

H.W

$$7 \quad (+259)_{10} = (?)_{10} = (?)_{2's} = (?)_9's$$

$$259 \div 2 \quad 1$$

$$129 \div 2 \quad 1$$

$$64 \div 2 \quad 0$$

$$32 \div 2 \quad 0$$

$$16 \div 2 \quad 0$$

$$8 \div 2 \quad 0$$

$$4 \div 2 \quad 0$$

$$2 \div 2 \quad 0$$

$$1 \div 2 \quad 1$$

$$\therefore (259)_{10} = (01000000011)_2 = (1011111100)_2 = 00100101$$

Now, convert it into 2's complement

To convert it into 2's complement add 1 from L

$$\begin{array}{r}
 & 1 & 0 & 1 & 1 & 1 & 1 & 1 & 0 & 0 \\
 + & & & & & & & & & \\
 \hline
 & 1 & 0 & 1 & 1 & 1 & 1 & 1 & 0 & 1
 \end{array}$$

$$(2) \quad \therefore (259)_{10} = (1011111101)_2$$

$$\rightarrow (259)_{10} = (?)_9's$$

$$\begin{array}{r}
 & 9 & 9 & 9 \\
 - & 2 & 5 & 9 \\
 \hline
 & 7 & 4 & 0
 \end{array}$$

$$\therefore (259)_{10} = (740)_9's$$

2] $(74)_{10} = (?)_1's = (?)_2's = (?)_9's$

$$\begin{array}{r}
 74 \div 2 & 0 \\
 37 \div 2 & 1 \\
 18 \div 2 & 0 \\
 9 \div 2 & 0 \\
 4 \div 2 & 0 \\
 2 \div 2 & 0 \\
 0 & 1
 \end{array}$$

$$\therefore (74)_{10} = (00101001) = (11010110)_1's$$

Now, convert it into 2's complement

To convert $(11010110)_1's$ in 2's complement add 1
from LSB

$$\begin{array}{r}
 11010110 \\
 + \quad \quad \quad 1 \\
 \hline
 11010111
 \end{array}$$

$$\therefore (74)_{10} = (11010111)_2's$$

$$\rightarrow (74)_{10} = (?)_9's$$

$$\begin{array}{r}
 9 \ 9 \ 0 \\
 - 7 \ 4 \\
 \hline
 2 \ 5
 \end{array}$$

$$\therefore (74)_{10} = (25)_9's$$

Rule :-

	Sum	Carry	Result
0	0	0	0
0 0	0	0	0
0 1	1	0	1
1 0	1	0	1
1 1	0	1	10

$$\begin{array}{r}
 1 \\
 + 01101 \\
 \hline
 100010
 \end{array}$$

$$\begin{array}{r}
 1 \\
 + 101101 \\
 \hline
 10000101
 \end{array}$$

$$\begin{array}{r}
 1 \\
 + 111001 \\
 \hline
 101011
 \end{array}$$

- Even no 1's in column the result is 0.
- Odd no 1's in column the result is 1.

Binary Arithmetic

7 Addition

21 Subtraction

3] Multiplication

4] Division

Subtraction

A	B	Diff	Borrow	
0	0	0	0	1 0 1 1 0
0	1	1	1	0 1 0 0 0
1	0	1	0	
1	1	0	0	1 1 1 1 1

$$\begin{array}{r} \boxed{1} & 1 & 1 & 0 & 1 \\ - & 0 & 1 & 1 & 1 \\ \hline 0 & 1 & 1 & 0 \end{array}$$

$$\begin{array}{r}
 & 10 & 10 & 1 & 1 & 0 \\
 \text{B} & 1010 & 101 & 11 & 01 \\
 - & 1001 & 110 & 101 & 01 \\
 \hline
 & 0000 & 111 & 010 & 00
 \end{array}$$

$$\begin{array}{r} 2] \quad 1 \ 0 \ 0 \ 1 \\ - \ 0 \ 1 \ 1 \ 1 \\ \hline 0 \ 0 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} 101110.11 \\ - 100110.10 \\ \hline 000110.10 \end{array}$$

$$\begin{array}{r} \text{57} \\ \hline -00001 \\ \hline 10006 \end{array}$$

0100011
1000110

0111.10 29 flwyr wt annulos ni 2' on new
· 1 29 flwyr snt annulos ni 2' on bl

Multiplication

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

$$\begin{array}{r} 1010 \\ \times 101 \\ \hline \end{array}$$

$$\begin{array}{r} 1010 \\ 0000 \\ + 1010 \\ \hline 100010 \end{array}$$

Division

01 → quotient

$$\begin{array}{r} 101 \\ 11 \overline{)101} \\ -0 \\ \hline 101 \\ 11 \\ \hline 10 \end{array}$$

10 → Remainder

$$\begin{array}{r} 0 \\ 110 \\ 111 \overline{)110} \\ \underline{-111} \\ 0 \\ 110 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 10 \overline{)110} \\ 0-10 \\ \hline 010 \\ 01 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 1 \\ 101 \overline{)101} \\ -101 \\ \hline 010 \\ 01 \\ \hline 0 \end{array}$$

→ Boolean Algebra

Boolean Algebra is a system of mathematical logic any & complex statement can be expressed by boolean function

The boolean algebra is governed by certain well developed rules and laws.

The binary digits 0 and 1 are used to represent the 2 voltage levels

Binary 1 represent the higher of 2 voltage levels i.e. 5V and binary 0 represent the lower of 2 voltage level i.e. 0V

In boolean algebra the multiplication and addition of the variables and function are also only logical

logical multiplication is the same as a AND operation and logical addition is same as OR operation

Definition of Boolean algebra:

It is the set of rule used to simplify the given logic expression without changing its functionality. It is used when number of variables are less.

logic operations:

- 1] AND, OR, and NOT are the 3 basic operations or functions that are performed in boolean algebra.
- 2] In addition there are some derived operations such as NAND, NOR, X-OR and X-NOR that are also performed in boolean algebra.

AND operation: The AND operation in boolean algebra is similar to multiplication in ordinary algebra in fact it is logical multiplication as performed by the AND gate.

Boolean laws

1 Complementation law

UNIT - 2

Boolean laws

1] Complementation law

1. $0 = 1$
2. $\bar{1} = 0$
3. If $A = 0$ then $\bar{A} = 1$
4. If $A = 1$ then $\bar{A} = 0$
5. $\bar{\bar{A}} = A$

2] AND law

1. $A \cdot 0 = 0$
2. $A \cdot 1 = A$
3. $A \cdot A = A$
4. $A \cdot \bar{A} = 0$
- 5.

3] OR law

1. $A + 0 = A$
2. $A + 1 = 1$
3. $A + A = A$
4. $A + \bar{A} = 1$

4] Commulative law

$$A+B = B+A$$

$$A \cdot B = B \cdot A$$

5] Idempotency law

$$A \cdot A = A$$

$$A+A = A$$

6] Transposition law

$$AB + \bar{A}C = (A+C)(\bar{A}+B)$$

7] The Associative law

The Associative law allow grouping of variable . There are 2 associative law



$$\text{aw1 } (A+B)+C = A+(B+C)$$

$$\text{aw2 } (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

In law 1 A OR B ORed with C is same that in A ordered with B OR C .

This law states that the way the variables are grouped and ORed is immaterial.

Logic diagram:

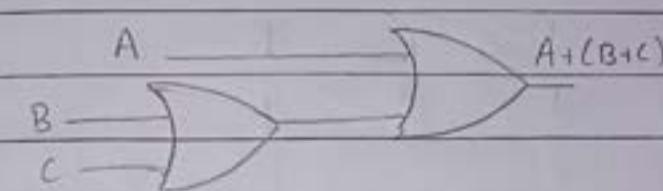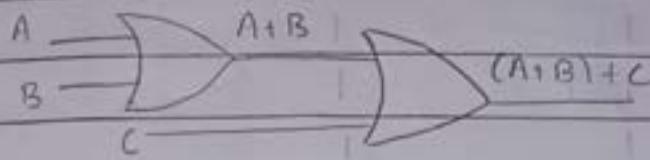

$$(A+B)+C = A+(B+C)$$

Truth table

A	B	C	$A+B$	$(A+B)+C$	Shows
0	0	0	0	0	
0	0	1	0	0	
0	1	0	1	1	=
0	1	1	1	1	
1	0	0	1	1	
1	0	1	1	1	
1	1	0	1	1	
1	1	1	1	1	


A	B	C	$(B+C)$	$A+(B+C)$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

o Law 2: $(A \cdot B) \cdot C = A \cdot (B \cdot C)$


A and B ANDed with C same as A ANDed with B and C

This law states that the way the variables are grouped and ANDed is immaterial.

logic diagram

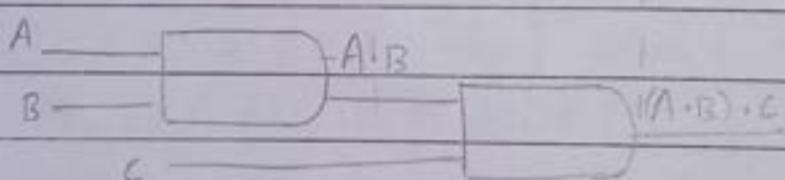

=

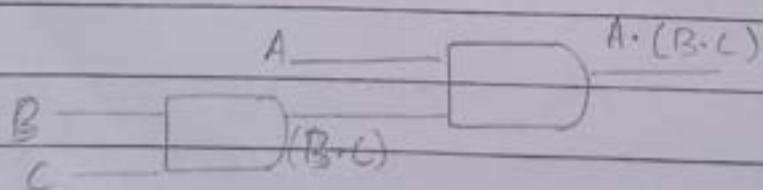

Truth table

A B C	$A \cdot B$	$(A \cdot B) \cdot C$		A B C	$B \cdot C$	$A \cdot (B \cdot C)$
0 0 0	0	0		0 0 0	0	0
0 0 1	0	0		0 0 1	0	0
0 1 0	0	0		0 1 0	0	0
0 1 1	0	0	=	0 1 1	1	0
1 0 0	0	0		1 0 0	0	0
1 0 1	0	0		1 0 1	0	0
1 1 0	1	0		1 1 0	0	0
1 1 1	1	1		1 1 1	1	1

$$(A \cdot B) \cdot C \cdot D = (A \cdot B \cdot C) \cdot D = (A \cdot B) \cdot (C \cdot D)$$


8] Distributive law

This distributive law allow factoring or multiplying out of expressions. So there are 3 distributive laws:

$$\text{law 1: } A(B+C) = AB + BC$$

This law states that ORing of several variables and ANDing the result with a singal variable is equivalent to ANDing that singal variable with all the several variables and then ORing the products.

logic diagram :

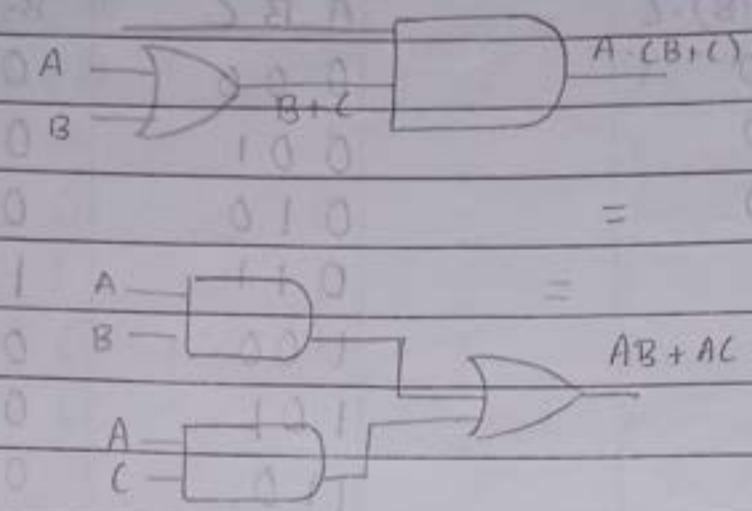

This law applies to singal variable as well as combination of variable

$$\text{Ex: } ABC(D+E) = ABCD + ABCE$$

$$\therefore AB(CD+EF) = ABCD + ABGF$$

The distributive property is often use in the reverse that is $AB + BC$ replace by $A(B+C)$ and $ABC + ABD$ replaced by $A B(C+D)$

This law states that ANDing of several variables and ORing the result with a singal variable is equivalent to ORing that singal variable with each of the several variables and then ANDing the sums. This can be proved algebraically or by truth table.

$$\text{law 2: } A + BC = (A+B)(A+C)$$

$$\text{law 3: } A + \bar{A}B = A + B$$

$$(A+B) (A+C)$$

$$= A \cdot A + AC + AB + BC$$

$$= A(1 + C + B) + BC$$

$$= A \cdot 1 + BC$$

$$= A + BC$$

A	B	C	$A+B+C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


$A \oplus B = A + B \cdot \bar{A} + \bar{B} + A \cdot \bar{B}$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0
1	0	1
1	1	0
0	1	1
0	0	0

Law 3: $A + \bar{A}B = A + B$

This law states that ORing of variable with AND of the variable complement of that variable with another variable is equal to ORing of 2 variables.
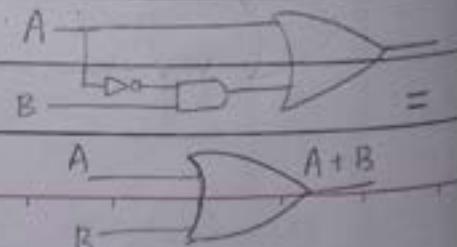
$$\begin{aligned}
 A + \bar{A}B &= (A + \bar{A})(A + \bar{B}) \\
 &= (A + B) \\
 &= A + B
 \end{aligned}$$



A	B	\bar{A}	$\bar{A}B$	$A + AB$		A	B	$A + B$
0	0	1	0	0	=	0	0	0
0	1	1	1	1	=	0	1	1
1	0	0	0	1	=	1	0	1
1	1	0	0	1	=	1	1	1

Demorgan's theorem : Demorgan's theorem represent 2 most powerful laws in Boolean Algebra.

Law 1 : $\overline{A+B} = \bar{A} \cdot \bar{B}$

This law states that compliment of sum of variables equals to the product of their individual compliment.

That is the compliment of 2 or more variables or together is same as the AND of compliments of each of the individual variables.



It shows that NOR gate equivalent to bubbled AND gate.

This law can be extended to any number of variables or combinations of variables, for example :

$$\overline{A+B+C+D} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} \dots$$

$$\overline{AB+CD+EF+AE} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} \cdot \bar{E} \cdot \bar{F} \cdot \bar{A} \cdot \bar{E} \dots$$

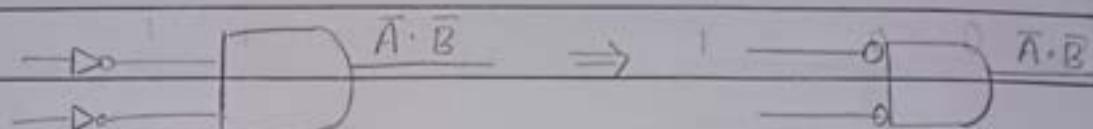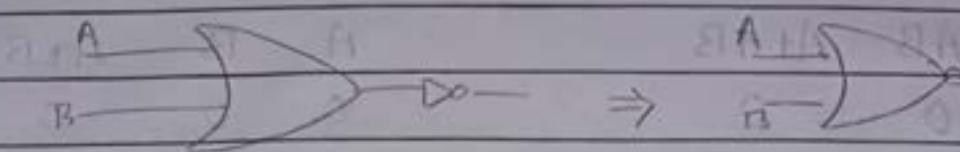This law permits individual removal of individual variable from a 'NOR' sign and transformation from a sum of product from (SOP) to a product of sums formed.



$$\begin{array}{cccc} A & B & A+B & \overline{A+B} \\ \hline 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 \\ 1 & 1 & 1 & 0 \end{array}$$

$$0 \quad 0 \quad 0 \quad 1$$

$$0 \quad 1 \quad 1 \quad 0$$

$$1 \quad 0 \quad 0 \quad 1$$

$$1 \quad 1 \quad 1 \quad 0$$

$$\begin{array}{ccc} A & B & \bar{A}\bar{B} \\ \hline 0 & 0 & 1 \\ 0 & 1 & 0 \\ 1 & 0 & 0 \\ 1 & 1 & 0 \end{array}$$

$$0 \quad 0 \quad 1$$

$$0 \quad 1 \quad 0$$

$$1 \quad 0 \quad 0$$

$$1 \quad 1 \quad 0$$

Q. Reduc $\overline{AB} + \overline{A} + AB$

$$= \overline{AB} \cdot \overline{A} \cdot \overline{AB} \overline{AB}$$

$$= AB \cdot A \cdot \overline{AB}$$

$$= AB \cdot \overline{AB}$$

$$\begin{aligned}
 2) & A [B + \bar{C} (\overline{AB} + A\bar{C})] \\
 = & A [B + \bar{C} (\overline{AB} \cdot \bar{A}\bar{C})] \\
 = & A [B + \bar{C} ((\bar{A} + \bar{B})(\bar{A} + C))] \\
 = & A [B + \bar{C} (A\bar{A} + \bar{A}C + \bar{B}\bar{A} + BC)] \\
 = & A [B + \bar{C} (\bar{A} + \bar{A}C + \bar{B}\bar{A} + \bar{B}C)] \\
 = & A [B + \bar{A}\bar{C} + \bar{A}C \cdot \bar{C} + \bar{B}\bar{A}\bar{C} + \bar{B}C \cdot \bar{C}] \\
 = & A [B + \bar{A}\bar{C} + 0 + \bar{A}\bar{B}\bar{C} + 0] \quad 1 + A = 1 \\
 = & A [B + \bar{A}\bar{C} (1 + \bar{B})] \\
 = & A [B + \bar{A}\bar{C}] \\
 = & AB + A \cdot \bar{A}\bar{C} \\
 = & AB + 0 \\
 = & AB
 \end{aligned}$$

$$\begin{aligned}
 3) & (\overline{A + \bar{B}C}) (A\bar{B} + ABC) \\
 = & (\bar{A} \cdot \bar{\bar{B}}\bar{C}) (A\bar{B} + ABC) \\
 = & (\bar{A} \cdot BC) (A\bar{B} + ABC) \\
 = & (\bar{A} \cdot BC) A (\bar{B} + BC) \\
 = & 0
 \end{aligned}$$

$$\begin{aligned}
 4) & (B + BC) (B + \bar{B}C) (B + D) \\
 = & BB + B\bar{B}C + BBC + \cancel{BC\bar{B}C} (B + D) \\
 = & B + 0 + BC + 0 (B + D) \\
 = & (B \cdot B + B\bar{B}C) (B + D) \\
 = & (B + 0) (B + D) \\
 = & B
 \end{aligned}$$

* Sum of product and product of sum

$$\rightarrow AB + AC$$

$$AB(C + \bar{C}) + AC(B + \bar{B})$$

$$ABC + ABC\bar{C} + ABC + A\bar{B}C$$

$$ABC + A\dot{B}\dot{C} + A\dot{B}\dot{C}$$

1 6 5

$$\Sigma M(5, 6, 7)$$

$$\rightarrow ABC + A\bar{C}D + CD$$

$$ABC(D + \bar{D}) + A\bar{C}D(B + \bar{B}) + CD(A + \bar{A})(B + \bar{B})$$

$$ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}\bar{C}D + ACD(B + \bar{B}) + \bar{A}CD(B + \bar{B})$$

$$ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}\bar{C}D + \cancel{ACD(B + \bar{B})}^{ABCD} + A\bar{B}CD + \bar{A}BCD + \bar{A}\bar{B}CD$$

D C 9 A 9 B F 7 3

$$\Sigma M(3, 7, 9, B, C, D, F)$$

* Boolean function & their representation

Function of 'n' boolean variable denoted by $F(x_1, x_2, \dots, x_n)$ is another variable of algebra and takes one of the 2 possible values 0 & 1 the variable ways of representing given function are :

- 1] Sum of product (SOP) form
- 2] Product of Sum (POS) form
- 3] Standard SOP form / Canonical SOP form
- 4] Standard POS form / Canonical POS form

1] SOP:

This form is also called disjunctive normal form.

$$\text{Ex: } f(A, B, C) = \bar{A}B + \bar{B}C$$

2] POS:

This form is also called conjunctive normal form.

$$\text{Ex: } f(A, B, C) = (\bar{A} + \bar{B})(B + C)$$

3] Standard SOP form:

This form is also called as disjunctive canonical form also it is called expanded SOP form or canonical SOP form. In this form function is sum of a number of product terms where each product term contains all the variable of the function either in complimented form. A product term which contains all the variable of the function either in complimented or uncomplimented form is called minterm. A minterm assume the value 1 only for 1 combination of the variable. An 'n' variable function can have at the most 2^n minterms. The sum of minterm whose value is equal to 1 is the standard sum of the product form of the function. The minterm denoted as m_0, m_1, \dots, m_n where suffixes are the decimal code of the combinations

$$\begin{aligned} & \bar{A}B + \bar{B}C \\ &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C} \\ &= m_3 + m_2 + m_5 + m_1 \\ &= \sum m(1, 2, 3, 5) \end{aligned}$$

Where $\sum m$ represents all the minterms whose element denoted decimal term is given in parenthesis.

4] Standard POS form:

This is called conjunctive canonical form. It is also called conjunctive expanded POS form or canonical POS form. This derived by considering the combination form which $f=0$. Each term is the sum of all the variable. A variable appears in uncomplimented form if it has a value of 0 in the combination and appears in complimented form if it has a value of 1 in the combination.

$$\begin{aligned}
 f(A, B, C) &= (\bar{A} + \bar{B})(B + C) \\
 &= (\bar{A} + \bar{B} + C\bar{C})(A\bar{A} + B + C) \\
 &= (\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})(A + B + C)(A + B + C) \\
 &= 6 \cdot 7 \cdot 0 \cdot 4 \\
 &= \Pi M(0, 4, 6, 7)
 \end{aligned}$$

A sum terms which contains each of the 1 variable in either complimented or uncomplimented form.

A maxterm assume the value 0 only for the 1 combination it will be 1. There will be at the most 2^n maxterms.

$$\text{Q. } A(\bar{B}+A)B$$

$$= \cancel{A\bar{B}B+AAAB} (A+B\bar{B}) (A+\bar{B}) \cdot (B+A\bar{A})$$

$$= (A+B) (A+\bar{B}) (A+\bar{B}) (A+B) (\bar{A}+B)$$

$$= (A+B) (A+\bar{B}) (\bar{A}+B)$$

$$= M_0 \cdot M_2 \cdot M_1$$

$$= \prod M(0, 1, 2)$$

$$\text{Q. } F(A, B, C) = (AB+C) (AC+B) \rightarrow \text{in POS}$$

$$= (A+C) (\cancel{B+C}) (A+B) (C+B)$$

$$= (A+C) (A+B) (C+B)$$

$$= (A+B+C) (A+\bar{B}+C) (\cancel{A+B+C}) (\cancel{A+B+C}) (\cancel{A+B+C})$$

$$(\bar{A}+B+C)$$

$$= (A+B+C) (A+\bar{B}+C) (A+B+\bar{C}) (\bar{A}+B+C)$$

$$= M_0 \cdot M_2 \cdot M_1 \cdot M_4$$

$$= \prod M(0, 2, 2, 4)$$

$$\text{Q. } F(A, B, C) = (AB+C) (AC+B) \rightarrow \text{in SOP}$$

$$= AB \cdot AC + AB \cdot B + CA \cdot C + C \cdot B$$

$$= ABC + AB\bar{C} + AC\bar{B} + CB$$

$$= ABC + ABC + ABC + ABC + A\bar{B}C + A\bar{B}\bar{C} + \cancel{ABC} + \cancel{ABC}$$

$$= M_2 + M_6 + M_5 + M_3$$

$$= \sum m(3, 5, 6, 7)$$

$$\text{Q. } \prod F = \bar{B}D + \bar{A}D + BD$$

~~$$= \bar{B}DA + \bar{B}D\bar{A} + \bar{A}DB + \bar{A}D\bar{B} + BCA + BC\bar{A}$$~~

~~$$= \bar{B}D\bar{A}C + A\bar{B}CD + A\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D +$$~~

~~$$\bar{A}B\bar{C}D + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + ABCD + ABC\bar{D} + \bar{A}BC\bar{D} + \bar{A}B\bar{C}\bar{D}$$~~

~~$$= M_1 + M_2 + M_3 + M_4 + M_5$$~~

$$\begin{aligned}
 2] \quad F &= AB + A\bar{C} \\
 &= ABC + ABC + A\bar{B}\bar{C} + A\bar{B}C \\
 &= M_7 + M_6 + M_4 \\
 &= \Sigma m(4, 6, 7) \\
 &= \Pi M(0, 1, 2, 3, 5)
 \end{aligned}$$

$$\begin{aligned}
 3] \quad F &= A(\bar{A} + B)(\bar{A} + B + \bar{C}) \\
 &= (\bar{A} + B)(A + \bar{B})(\bar{A} + B + C) + (\bar{A} + B + \bar{C})(\bar{A} + B + C) \\
 &= (\bar{A} + B + C)(A + B + \bar{C})(A + \bar{B} + C) \cancel{(A + \bar{B} + \bar{C})} (\bar{A} + B + C) \\
 &\quad (\bar{A} + B + \bar{C})(\bar{A} + B + C) \\
 &= \Pi M(0, M_0, M_1, M_2, M_4, M_5, M_3) \\
 &= \Pi M(0, 1, 2, 4, 5) \\
 &= \Sigma m(0, 6, 7)
 \end{aligned}$$

$$\begin{aligned}
 1] \quad F &= \bar{B}D + \bar{A}D + BD \\
 &= A\bar{B}D + \bar{A}\bar{B}D + \bar{A}BD + \cancel{\bar{A}\bar{B}D} + ABD + \cancel{\bar{A}BD} \\
 &= M_5 + M_1 + M_3 + M_7 \\
 &= \Sigma m(1, 3, 5, 7)
 \end{aligned}$$

- K map is up to only 6 variables
- No. of cells = 2^6
- Only adjacent elements can form group
- Diagonal element can not form group

Page No. _____

Date _____

Unit 3:Combination Logic and Combinational Circuit

* Karnaugh map

2-variable

→ SOP

A	B	\bar{B}	B
0	0	1	1
1	1	0	0
A	2	3	3

$$\bar{A}\bar{B} + \bar{A}B = \bar{A}(\bar{B} + B)$$

$$F = \bar{A}$$

→ POS

A	B	\bar{B}	B
0	0	1	1
1	1	0	0
\bar{A}	2	3	3

$$F = (A+B)(A+\bar{B}) = A$$

3-variable

SOP

A	BC	00	01	11	10
	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC	
0	0	1	3	2	
1	4	5	7	6	

$$\left. \begin{array}{l} \\ \end{array} \right\} Y_1 C_1 + Y_2 C_2$$

POS

A	BC	00	01	11	10
	$B+C$	$B+\bar{C}$	$\bar{B}+\bar{C}$	$\bar{B}+C$	
0	0	1	3	2	
1	4	5	7	6	

$$\left. \begin{array}{l} \\ \end{array} \right\} (Y_1 + G_1)(Y_2 + G_2)$$

$$\Sigma m(0, 2, 3, 4, 5, 6)$$

$$\Pi M (0, 1, 2, 3, 4, 7)$$

Q

	$\bar{B}C$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
$A \backslash$	$\bar{A}0$	1		1	1
A_1	1	1		1	1

$\left. \begin{array}{l} \\ \end{array} \right\} \gamma_1 C_1 + \gamma_2 C_2$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C}$$

$$\bar{B}\bar{C}(\bar{A}+A) + B\bar{C}(A+\bar{A})$$

$$\bar{B}\bar{C} + B\bar{C}$$

$$(\bar{B}+B)\bar{C}$$

$$\bar{C}$$

$$F = \bar{C} + A\bar{B} + \bar{A}B$$

Q

	$B+C$	$B+\bar{C}$	$\bar{B}+\bar{C}$	$\bar{B}+C$
$A \backslash$	0	1	2	3
A_1	0	1	0	1

$\downarrow B+C \quad \downarrow B+\bar{C}$

$$F = A \cdot (B+C) (\bar{B}+\bar{C})$$

Q

$$F(P, Q, R) = \sum m(0, 1, 3, 5, 7)$$

Q

	$\overline{P}R$	$\overline{P}\overline{R}$	PR	$P\overline{R}$	$P\bar{R}$
$P \backslash$	0	1	2	1	3
P_1	4	5	1	7	6

$\left. \begin{array}{l} \\ \end{array} \right\} \gamma_1 C_1 + \gamma_2 C_2$

$$F(A, B, C) = \prod M(1, 2, 4, 6)$$

$$F(A, B, C) = \sum m(1, 2, 4, 5, 7)$$

$$F(A, B, C) = \sum m(1, 2, 4, 5, 7)$$

Reduce the following expression by, using K-map

$$1] AB + A\bar{B}C + \bar{A}\bar{B}C + BC$$

$$= ABC + ABC + A\bar{B}C + \bar{A}\bar{B}C + A\bar{B}C + \bar{ABC}$$

$$= 0 + 7 + 6 + 5 + 0 + 2 m_7 + m_6 + m_5 + m_2$$

$$= \sum m(0, 2, 5, 6, 7, 11) (m_2, m_5, m_6, m_7)$$

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
0 0	0	1	1	0
0 1	1	1	1	1
1 0				
1 1				

$$AB\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$= AC + BC$$

$$2] (A+B)(A+\bar{B}+C)(A+\bar{C})$$

$$= (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(A+\bar{B}+\bar{C})$$

$$= 0 \cdot 1 \cdot 2 \cdot 3 M_0 \cdot M_1 \cdot M_2 \cdot M_3$$

$$= \prod M(M_1, M_2, M_3, M_0)$$

A \ B+C	$\bar{B}+C$	$B+\bar{C}$	$B+\bar{C}$	$\bar{B}+C$
0 0	0	1	1	0
0 1	1	0	1	1
1 0				
1 1				

$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})(A+\bar{B}+C)$$

$$= (A+B)(A+\bar{B})$$

$$= A$$

* 4 variable K-map

SOP

		$\bar{C}D$	$\bar{C}D$	$\bar{C}D$	CD	$C\bar{D}$
		00	01	11	10	01
$\bar{A}\bar{B}$		0	1	3	2	
$\bar{A}\bar{B}$	01	4	5	7	6	
$A\bar{B}$	11	12	13	15	14	
$A\bar{B}$	10	8	9	11	10	

POS

		$\bar{C}D$	$C\bar{D}$	$\bar{C}D$	$C\bar{D}$	$\bar{C}D$
		00	01	11	10	01
$A+B$		0	1	3	2	
$A+\bar{B}$	01	4	5	7	6	
$\bar{A}+\bar{B}$	11	12	13	15	14	
$\bar{A}+B$	10	8	9	11	10	

possible combinations of $ABCD = 8$, 11 , 14

Q. $\sum m(0, 1, 2, 6, 13, 15)$

		$\bar{C}D$	$\bar{C}D$	CD	CD	$C\bar{D}$
		00	01	11	10	01
$\bar{A}\bar{B}$		0	1	3	2	
$\bar{A}\bar{B}$	01	4	5	7	6	
$A\bar{B}$	11	12	13	15	14	
$A\bar{B}$	10	8	9	11	10	

$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}CD + ABCD$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}C\bar{D} + ABD$$

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}C\bar{D} + ABD$$

Q $\Sigma m(3, 7, 11, 12, 14)$

$AB \backslash CD$	CD	$\bar{C}D$	$\bar{C}\bar{D}$	CD	$C\bar{D}$
$AB \backslash$	00	01	11	10	01
$\bar{A}B\bar{A}B$	0	1	1	?	?
$\bar{A}B\bar{A}B$	4	5	17	6	
$A\bar{B}\bar{A}B$	12	13	15	16	
$A\bar{B}A\bar{B}$	8	9	11	10	

$$\bar{A}\bar{B}CD + A\bar{B}CD + ABC\bar{D} + ABCD + A\bar{B}CD$$

$$\bar{A}B\bar{C}D + ABD + A\bar{B}CD$$

Q $\Pi M(5, 7, 6, 9, 11, 14)$

$AB \backslash CD$	CD	$C\bar{D}$	$\bar{C}\bar{D}$	$\bar{C}D$	$\bar{C}+D$
$AB \backslash$	0	1	2	2	
$A+B$	0				
$A+\bar{B}$	4	15	17	16	
$\bar{A}+\bar{B}$	12	13	15	14	
$\bar{A}+B$	8	9	11	10	

($A+B+\bar{D}$) ($\bar{A}+B+\bar{D}$)

($\bar{A}+B+\bar{D}$)

$$AB + A\bar{C} + C + AD + A\bar{B}C + ABC$$

$$AB\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}\bar{C} + A$$

$$A + \bar{A}C + ABC\bar{D}$$

$$(A+\bar{B}+\bar{D})(\bar{A}+B+\bar{D})(B+\bar{C}+D)$$

$$AB + A\bar{C} + C + AD + A\bar{B}C + ABC$$

$$AB\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}\bar{C} + A$$

$$A + \bar{A}C + ABC\bar{D}$$

M.V Reduce by using K-map

$$i) AB + AC + C + AD + A\bar{B}C + ABC$$

$$AB\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + A\bar{B}\bar{C} + A$$

$$A + \bar{A}C + ABC\bar{D}$$

$$= ABC + AB\bar{C} + ABC + A\bar{B}\bar{C} + ABD + A\bar{B}D + A\bar{B}CD + A\bar{B}C\bar{D} + ABCD +$$

$$= ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD +$$

$$= ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD +$$

$$= ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD +$$

$$= ABCD + ABC\bar{D} + ABC\bar{D} + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD + A\bar{B}CD +$$

$$= \Sigma m_{15} + m_{14} + m_{12} + m_{13} + m_9 + m_3 + m_{11} + m_{10} + m_1 + m_6 + m_5 + m_2$$

Q) Reduce the expression

$\sum m(0, 2, 3, 4, 5, 6)$ using K-map and implement it in AOT logic as well as in NAND logic



	$\bar{A} \bar{B} C$	$\bar{B} \bar{C}$	$\bar{B} C$	$B \bar{C}$	$B C$
\bar{A}	0	1	1	1	1
A	1	1	0	0	0



$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A B\bar{C}$$

$$\bar{B}\bar{C} + B\bar{C}$$

$$F = \bar{C} + A\bar{B} + \bar{A}B$$

Not \rightarrow Nand

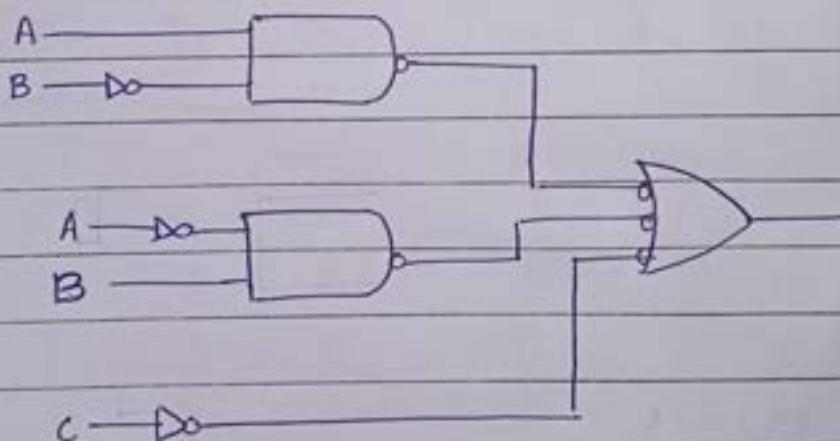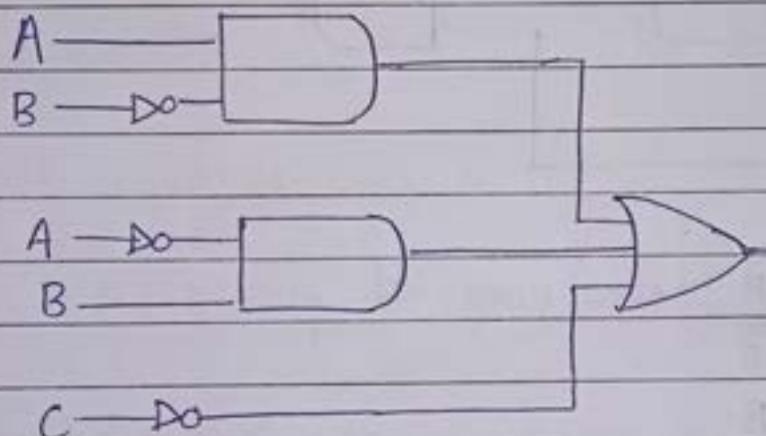

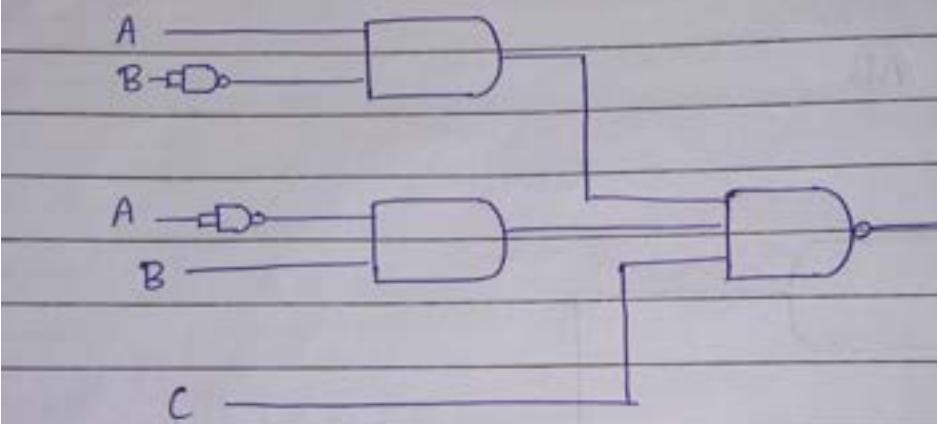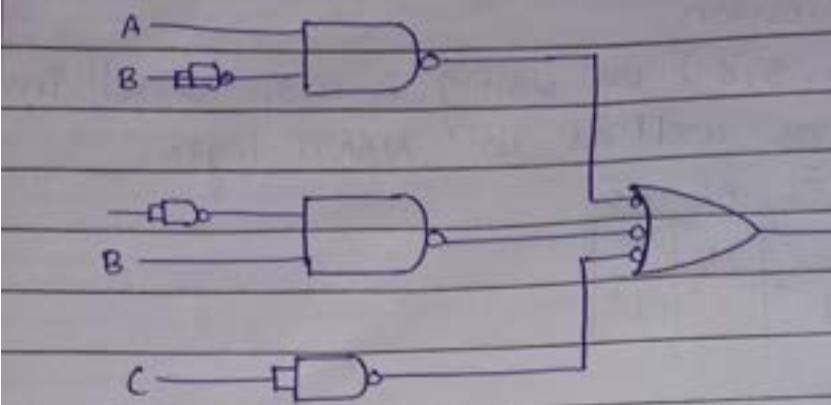

$$\text{C. } \bar{A} \cdot \bar{B} \cdot \bar{A} \cdot B$$

$$= \bar{C} + \bar{A} \cdot \bar{B} + \bar{A} \cdot B$$

$$= \bar{C} + A \cdot \bar{B} + \bar{A} \cdot B$$

Q. $\sum m(0, 3, 4, 6) + d(1, 5)$

$A \backslash BC$	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	1	2
A	1	0	X	1

$$F = \bar{B} + A\bar{C} + \bar{A}C$$

Q. $\sum m(0, 1, 4, 5) + d(3, 7)$

	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
\bar{A}	0	1	X	2
A	1	0	X	1

$$F = \bar{B}$$

Code Converters

4 bit binary to gray code converter

Conversion table

	I/P 4 bit binary		O/P Gray code
	B_4 B_3 B_2 B_1	G_4 G_3 G_2 G_1	
0	0 0 0 0	0 0 0 0	
1	0 0 0 1	0 0 0 1	
2	0 0 1 0	0 0 1 1	
3	0 0 1 1	0 0 1 0	
4	0 1 0 0	0 1 1 0	
5	0 1 0 1	0 1 1 1	
6	0 1 1 0	0 1 0 1	
7	0 1 1 1	0 1 0 0	

	B_4	B_3	B_2	B_1	G_4	G_3	G_2	G_1
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

$$G_4 = \sum m (8, 9, 10, 11, 12, 13, 14, 15)$$

$$G_3 = \sum m (4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_2 = \sum m (2, 3, 4, 5, 10, 12, 13)$$

$$\nabla^{\oplus} G_1 = \sum m (1, 2, 5, 6, 9, 10, 13, 14)$$

→ For G_4

$\cancel{B_2 B_1}$	$B_4 B_3$	$\bar{B}_2 \bar{B}_1$	$\bar{B}_2 B_1$	$B_2 B_1$	$\bar{B}_2 \bar{B}_1$
$\bar{B}_4 \bar{B}_3$	0	1	3	2	
$\bar{B}_4 B_3$	4	5	7	6	
$B_4 B_3$	1 ¹²	1 ¹³	1 ¹⁵	1 ¹⁴	
$B_4 \bar{B}_3$	1 ⁵	1 ⁷	1 ¹¹	1 ¹⁰	

$$\begin{aligned}
 G_4 &= B_4 B_3 \bar{B}_2 \bar{B}_1 + B_4 B_3 \bar{B}_2 B_1 + \\
 &\quad B_4 B_3 B_2 \bar{B}_1 + B_4 B_3 B_2 B_1 + \\
 &\quad B_4 \bar{B}_3 \bar{B}_2 \bar{B}_1 + B_4 \bar{B}_3 \bar{B}_2 B_1 + \\
 &\quad B_4 \bar{B}_3 B_2 \bar{B}_1 + B_4 B_3 B_2 B_1
 \end{aligned}$$

$$\begin{aligned}
 G_4 &= B_4 B_3 \bar{B}_2 + B_4 B_3 B_2 + B_4 \bar{B}_3 \bar{B}_2 + B_4 \bar{B}_3 B_2 \\
 &= B_4 B_3 + B_4 \bar{B}_3 \oplus = B_4
 \end{aligned}$$

→ For G_3

$\cancel{B_2 B_1}$	$B_4 B_3$	$\bar{B}_2 \bar{B}_1$	$\bar{B}_2 B_1$	$B_2 B_1$	$\bar{B}_2 \bar{B}_1$
$\bar{B}_4 \bar{B}_3$	0	1	3	2	
$\bar{B}_4 B_3$	4	5	7	6	
$B_4 B_3$	1 ¹²	1 ¹³	1 ¹⁵	1 ¹⁴	
$B_4 \bar{B}_3$	1 ⁵	1 ⁷	1 ¹¹	1 ¹⁰	

$$\begin{aligned}
 G_3 &= \bar{B}_4 B_3 \bar{B}_2 \bar{B}_1 + \bar{B}_4 B_3 \bar{B}_2 B_1 + \bar{B}_4 B_3 B_2 \bar{B}_1 + \\
 &\quad \bar{B}_4 B_3 B_2 \bar{B}_1 + B_4 \bar{B}_3 \bar{B}_2 \bar{B}_1 + B_4 \bar{B}_3 \bar{B}_2 B_1 + B_4 \bar{B}_3 B_2 \bar{B}_1 + \\
 &\quad B_4 \bar{B}_3 B_2 B_1 + B_4 \bar{B}_3 B_2 \bar{B}_1 \\
 &= \bar{B}_4 B_3 \bar{B}_2 + \bar{B}_4 B_3 B_2 + B_4 \bar{B}_3 \bar{B}_2 + B_4 \bar{B}_3 B_2 \\
 &= B_4 B_3 + B_4 \bar{B}_3 = B_4 \oplus B_3
 \end{aligned}$$

$B_2B_1 \rightarrow \text{For } G_2$


B_4B_3	$\bar{B}_1\bar{B}_1$	\bar{B}_2B_1	B_1B_1	$B_2\bar{B}_1$
$\bar{B}_4\bar{B}_3$	0	1	3	2
\bar{B}_4B_3	4	5	7	6
B_4B_3	12	13	15	14
$B_4\bar{B}_3$	8	9	11	10

$$\begin{aligned}
 G_2 &= \bar{B}_4B_3\bar{B}_2\bar{B}_1 + \bar{B}_4B_3\bar{B}_2B_1 + B_4B_3\bar{B}_2\bar{B}_1 + B_4B_3\bar{B}_2B_1 + \bar{B}_4\bar{B}_2B_2B_1 + \\
 &\quad \bar{B}_4\bar{B}_2B_2\bar{B}_1 + B_4\bar{B}_3B_2B_1 + B_4\bar{B}_3B_2\bar{B}_1 \\
 &= \bar{B}_4B_3\bar{B}_2 + B_4B_3\bar{B}_2 + \bar{B}_4\bar{B}_3B_2 + B_4\bar{B}_3B_2 \\
 &= B_3\bar{B}_2 + \bar{B}_3B_2 = B_3 \oplus B_2
 \end{aligned}$$

B_2B_1	$\bar{B}_2\bar{B}_1$	\bar{B}_2B_1	B_2B_1	$B_2\bar{B}_1$
$\bar{B}_4\bar{B}_3$	0	1	3	2
\bar{B}_4B_3	4	5	7	6
B_4B_3	12	13	15	14
$B_4\bar{B}_3$	8	9	11	10

$$\begin{aligned}
 G_1 &= \bar{B}_4\bar{B}_2\bar{B}_2B_1 + \bar{B}_4B_2\bar{B}_2B_1 + B_4B_3\bar{B}_2B_1 + B_4\bar{B}_2\bar{B}_2B_1 + \bar{B}_4\bar{B}_2B_2\bar{B}_1 + \\
 &\quad \bar{B}_4B_3B_2\bar{B}_1 + B_4B_3B_2B_1 + B_4\bar{B}_3B_2\bar{B}_1 \\
 &= \bar{B}_4\bar{B}_2B_1 + B_4\bar{B}_2B_1 + \bar{B}_4B_3\bar{B}_1 + B_4B_3\bar{B}_1 = \bar{B}_2B_1 + B_2\bar{B}_1
 \end{aligned}$$

$$G_1 = B_2 \oplus B_1$$

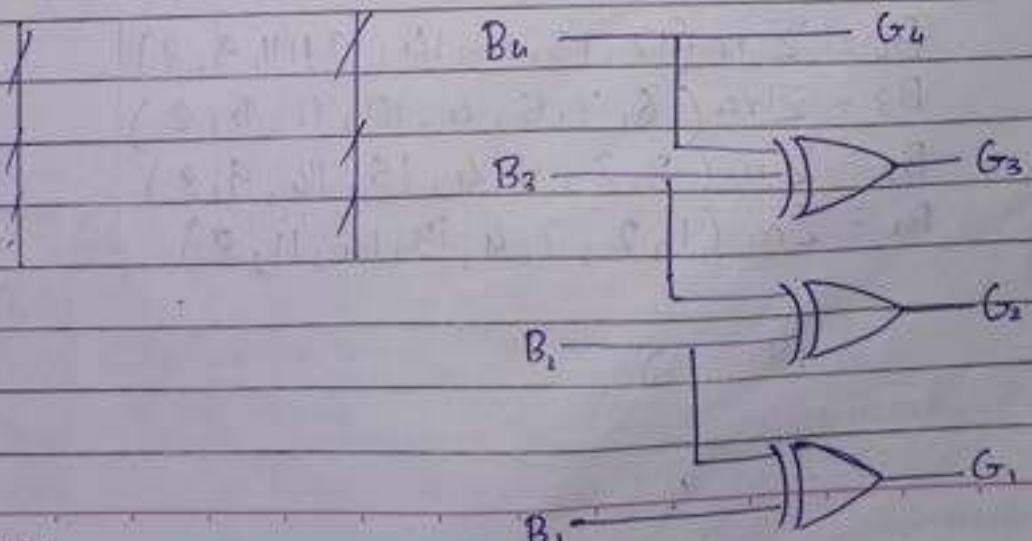

Design of a 4 bit gray to binary code converter
G to B

T/P				O/P			
G ₄	G ₃	G ₂	G ₁	B ₄	B ₃	B ₂	B ₁
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	1
3	0	0	1	1	0	0	1
2	0	0	1	0	0	1	1
6	0	0	1	0	1	0	0
7	0	1	1	1	0	1	0
5	0	1	0	1	0	1	0
4	0	1	0	0	0	1	1
12	1	1	0	0	1	0	0
13	1	1	0	1	1	0	0
15	1	1	1	1	0	1	0
14	1	1	1	0	1	0	1
10	1	0	1	0	1	1	0
11	1	0	1	1	1	1	0
9	1	0	0	1	1	1	0
8	1	0	0	0	1	1	1

$$B_4 = \sum m(12, 13, 15, 14, 10, 11, 9, 8)$$

$$B_3 = \sum m(6, 7, 5, 4, 10, 11, 9, 8)$$

$$B_2 = \sum m(3, 2, 5, 4, 15, 14, 9, 8)$$

$$B_1 = \sum m(1, 2, 7, 4, 13, 14, 11, 8)$$

→ For B_4

$\bar{B}_4 \bar{B}_3$	$\bar{B}_2 \bar{B}_1$	$\bar{B}_3 B_1$	$B_2 B_1$	$B_2 \bar{B}_1$
0	1	2	2	
4	5	7	6	
1	12	13	15	14
3	9	11	10	

$$\begin{aligned}
 B_4 &= B_4 B_3 \bar{B}_2 \bar{B}_1 + B_4 B_3 \bar{B}_2 B_1 + B_4 B_3 B_2 \bar{B}_1 + B_4 B_3 B_2 \bar{B}_1 + B_4 \bar{B}_3 \bar{B}_2 \bar{B}_1 + \\
 &\quad B_4 \bar{B}_3 \bar{B}_2 B_1 + B_4 \bar{B}_3 B_2 \bar{B}_1 + B_4 \bar{B}_3 B_2 \bar{B}_1 \\
 &= B_4 B_3 \bar{B}_2 + B_4 B_3 B_2 + B_4 \bar{B}_3 \bar{B}_2 + B_4 \bar{B}_3 B_2 = B_4 B_3 + B_4 \bar{B}_3
 \end{aligned}$$

=

→ For B_4

$G_2 G_1$

$G_4 G_3$	$\bar{G}_2 \bar{G}_1$	$\bar{G}_2 G_1$	$G_2 G_1$	$G_2 \bar{G}_1$
0	1	3	2	
4	5	7	6	
1	12	13	15	14
3	9	11	10	

$$\begin{aligned}
 B_4 &= G_4 G_3 \bar{G}_2 \bar{G}_1 + G_4 G_3 \bar{G}_2 G_1 + G_4 G_3 G_2 \bar{G}_1 + G_4 G_3 G_2 G_1 + \\
 &\quad G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1 + G_4 \bar{G}_3 \bar{G}_2 G_1 + G_4 \bar{G}_3 G_2 \bar{G}_1 + G_4 \bar{G}_3 G_2 G_1 \\
 &= G_4 G_3 \bar{G}_2 + G_4 G_3 G_2 + G_4 \bar{G}_3 \bar{G}_2 + G_4 \bar{G}_3 G_2 = G_4 G_3 + G_4 \bar{G}_3
 \end{aligned}$$

$$B_4 = G_4$$

→ For B_3

$G_4 G_3$	$\bar{G}_1 \bar{G}_2 \bar{G}_3 \bar{G}_4$	$\bar{G}_1 \bar{G}_2 \bar{G}_3 G_4$	$\bar{G}_1 \bar{G}_2 G_3 \bar{G}_4$	$\bar{G}_1 \bar{G}_2 G_3 G_4$
0	1	3	2	
4	5	7	1	6
1	12	13	15	14
3	9	11	10	

$$\begin{aligned}
 B_3 &= \bar{G}_4 G_3 \bar{G}_2 \bar{G}_1 + \bar{G}_4 G_3 \bar{G}_2 G_1 + \bar{G}_4 G_3 G_2 \bar{G}_1 + \\
 &\quad \bar{G}_4 G_3 G_2 G_1 + G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1 + G_4 \bar{G}_3 \bar{G}_2 G_1 + G_4 \bar{G}_3 G_2 \bar{G}_1 + \\
 &\quad G_4 \bar{G}_3 G_2 G_1 + G_4 \bar{G}_2 \bar{G}_3 \bar{G}_1 + G_4 \bar{G}_2 \bar{G}_3 G_1 + G_4 \bar{G}_2 G_3 \bar{G}_1 + \\
 &\quad G_4 \bar{G}_2 G_3 G_1 = \bar{G}_4 G_3 \bar{G}_2 + \bar{G}_4 G_3 G_2 + G_4 \bar{G}_3 \bar{G}_2 + G_4 \bar{G}_3 G_2 \\
 &= \bar{G}_4 G_3 + G_4 \bar{G}_3 = G_4 \oplus G_3
 \end{aligned}$$

→ For B_3




$\bar{G}_4 G_3$	$\bar{G}_4 \bar{G}_3$	$\bar{G}_3 G_1$	$G_1 G_2$	$G_2 \bar{G}_1$	$G_1 \bar{G}_2$
$\bar{G}_4 \bar{G}_3$	0	1	1	1	1
$\bar{G}_3 G_1$	1	0	3	2	6
$G_1 G_2$	12	13	15	14	
$G_2 \bar{G}_1$	18	9	11	10	

$$\begin{aligned}
 B_3 &= \bar{G}_4 \bar{G}_3 G_2 G_1 + \bar{G}_4 \bar{G}_3 G_1 \bar{G}_1 + \bar{G}_4 G_3 \bar{G}_2 \bar{G}_1 + \bar{G}_4 G_3 G_2 G_1 + G_4 G_3 G_2 \bar{G}_1 \\
 &\quad + G_4 G_3 G_2 \bar{G}_1 + G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1 + G_4 \bar{G}_3 G_2 G_1 \\
 &= \bar{G}_4 \bar{G}_3 G_2 + \bar{G}_4 G_3 \bar{G}_1 + G_4 G_3 G_2 + G_4 \bar{G}_3 \bar{G}_2 = f_4(G_4 \oplus G_3) + \\
 B_3 &= G_4 \oplus G_3 \oplus G_2
 \end{aligned}$$

→ For B_4

$\bar{G}_4 \bar{G}_3$	$\bar{G}_3 G_1$	$G_1 G_2$	$G_2 \bar{G}_1$
$\bar{G}_4 \bar{G}_3$	0	1	3
$\bar{G}_3 G_1$	1	4	5
$G_1 G_2$	12	13	14
$G_2 \bar{G}_1$	18	9	11

$$\begin{aligned}
 B_4 &= \bar{G}_4 \bar{G}_3 \bar{G}_2 G_1 + \bar{G}_4 \bar{G}_3 G_2 \bar{G}_1 + \bar{G}_4 G_3 \bar{G}_2 \bar{G}_1 + \bar{G}_4 G_3 G_2 G_1 + G_4 G_3 \bar{G}_2 G_1 + \\
 &\quad G_4 G_3 G_2 G_1 + G_4 \bar{G}_3 \bar{G}_2 \bar{G}_1 + G_4 \bar{G}_3 G_2 G_1 = G_4 \oplus G_3 \oplus G_2 \oplus G_1
 \end{aligned}$$

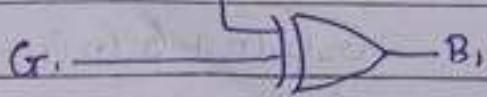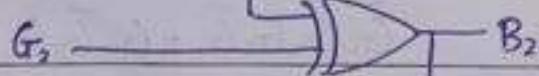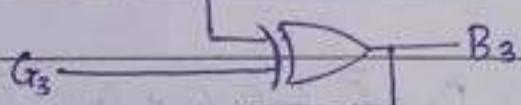 $G_4 \rightarrow B_4$ 

$$X_0 = B_4 + B_3 B_2 + B_3 B_1$$

$$Y_2 = \bar{B}_3 \bar{B}_2 \bar{B}_1 + \bar{B}_3 B_2 + \bar{B}_3 B_2$$

$$X_2 = \bar{B}_2 \bar{B}_1 + B_2 B_1 \quad \text{Page No. } \underline{\hspace{2cm}}$$

$$X_1 = \bar{B}_1 \quad \text{Date } \underline{\hspace{2cm}} / \underline{\hspace{2cm}}$$

H.U.
#

BCD to gray code converter.

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1

0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1


a 4-bit

Design of BCD to Ex-3 code converter

Encoder

Encoder is a device whose input are decimal digits or alphabetical characters whose output are the coded representation of those inputs i.e. an encoder is device which converts familiar no. or symbols into coded format.

M T/P

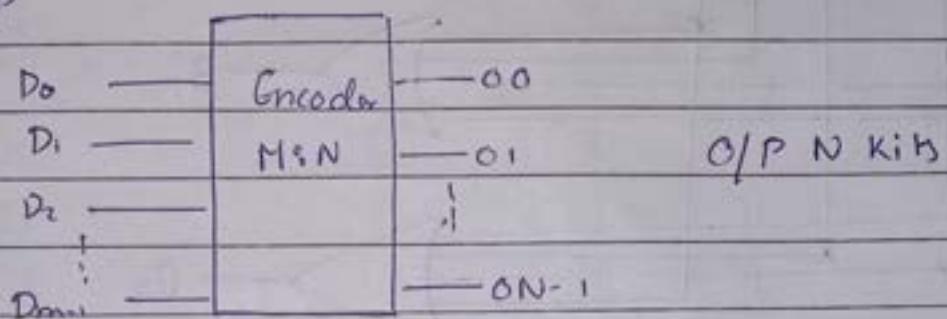

→ Octal to binary

Output I/P Binary O/P

D ₀	B ₂	B ₁	B ₀
----------------	----------------	----------------	----------------

D ₀	0	0	0
----------------	---	---	---

D ₁	0	0	1
----------------	---	---	---

D ₂	0	1	0
----------------	---	---	---


D ₃	0	1	1
----------------	---	---	---

D ₄	10	0	0
----------------	----	---	---

D ₅	1	0	1
----------------	---	---	---

D ₆	1	1	0
----------------	---	---	---

D ₇	1	1	1
----------------	---	---	---

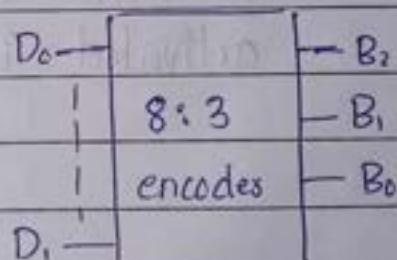


$$B_2 = D_4 + D_5 + D_6 + D_7$$

$$B_1 = D_2 + D_3 + D_6 + D_7$$

$$B_0 = D_1 + D_3 + D_5 + D_7$$

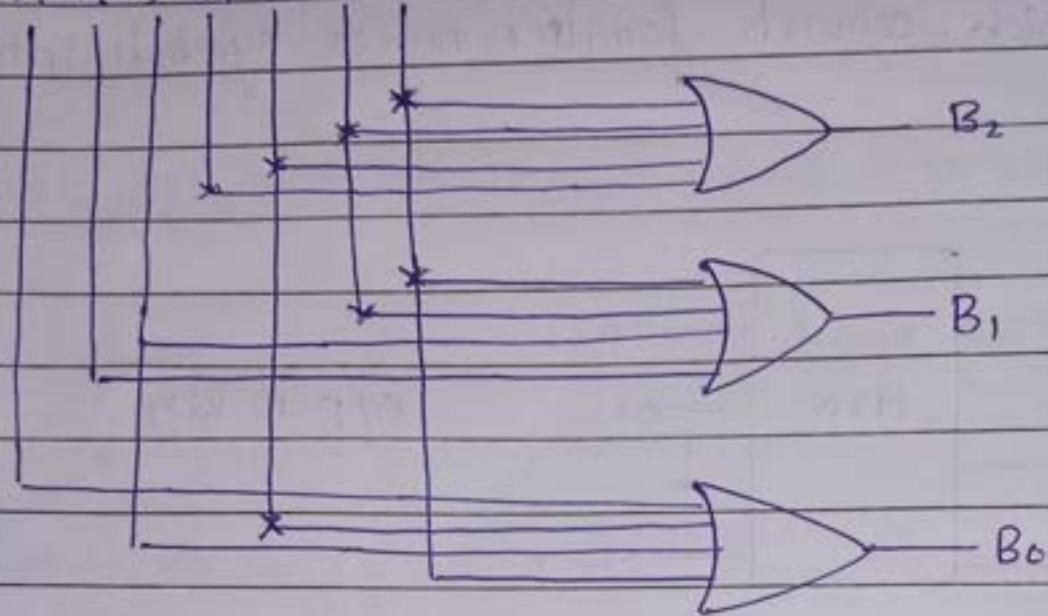$D_1 \ D_2 \ D_3 \ D_4 \ D_5 \ D_6 \ D_7$



An octal to binary encoder or 8 line to 3 line encoder accepts 8 input lines and produces to a three bit output code corresponding to the activated inputs.

→ Decimal to BCD encodes


Decimal I/P	B ₃	B ₂	B ₁	B ₀
D ₀	0	0	0	0
D ₁	0	0	0	1
D ₂	0	0	1	0
D ₃	0	0	1	1
D ₄	0	1	0	0
D ₅	0	1	0	1
D ₆	0	1	1	0
D ₇	0	1	1	1
D ₈	1	0	0	0
D ₉	1	0	0	1

$$B_3 = D_8 + D_9$$

$$B_2 = D_4 + D_5 + D_6 + D_7$$

$$B_1 = D_2 + D_3 + D_6 + D_7$$

$$B_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

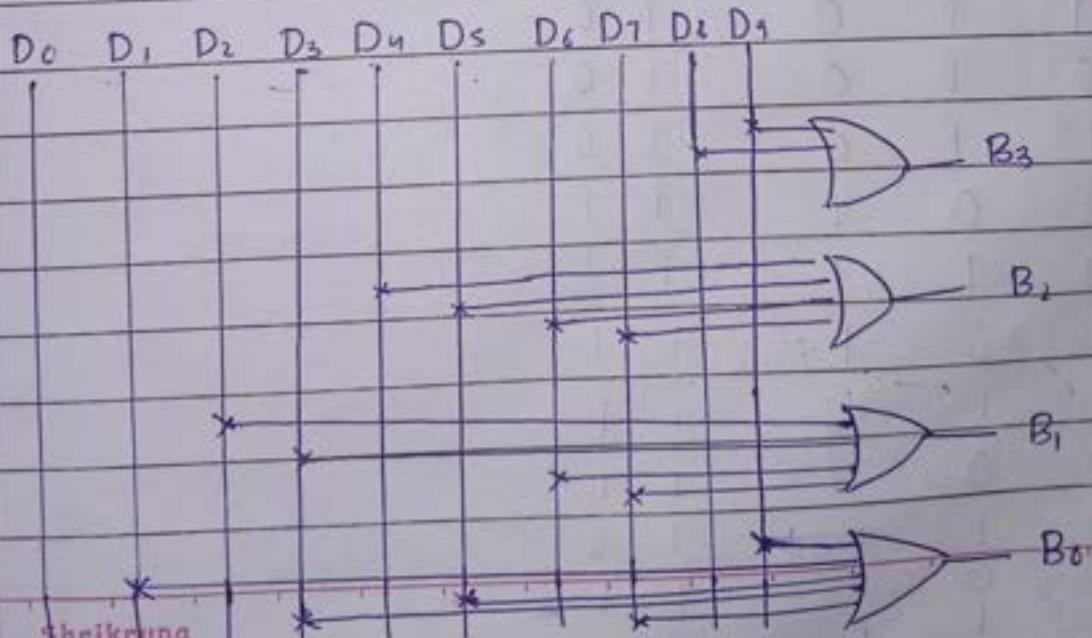

4 input Priority-Encoder

A priority encoder is a logic circuit that responds to just one input in accordance with some priority system. Among all those inputs may be simultaneous high.

4 I/P				O/P	
D ₀	D ₁	D ₂	D ₃	A	B
1	0	0	0	0	0
x	1	0	0	0	1
x	x	1	0	1	0
x	x	x	1	1	1

$$A = D_3 + B \bar{D}_3 D_2$$

$$B = D_3 + D_1 \bar{D}_2 \bar{D}_3$$

$$= D_3 + D_1 \bar{D}_2$$

→ Octal to Binary


	D ₀	D ₁	D ₂	D ₃	A	B
8	0	1	0	0	0	0
4	0	1	0	0	0	1
12	1	1	0	0	0	1
2	0	0	1	0	1	0
6	0	1	1	0	1	0
10	1	0	1	0	1	0
14	1	1	1	0	1	0
1	0	0	0	1	1	1
3	0	0	1	1	1	1
5	0	1	0	1	1	1
7	0	1	1	1	1	1
9	1	0	0	1	1	1
11	1	0	1	1	1	1
13	Shrikarpal	0	1	1	1	1
15	1	1	1	1	1	1

$$A = \Sigma m(2, 6, 10, 14, 1, 3, 5, 7, 9, 11, 13, 15)$$

$$B = \Sigma m(4, 12, 1, 3, 5, 7, 9, 11, 13, 15)$$

6

Encoders

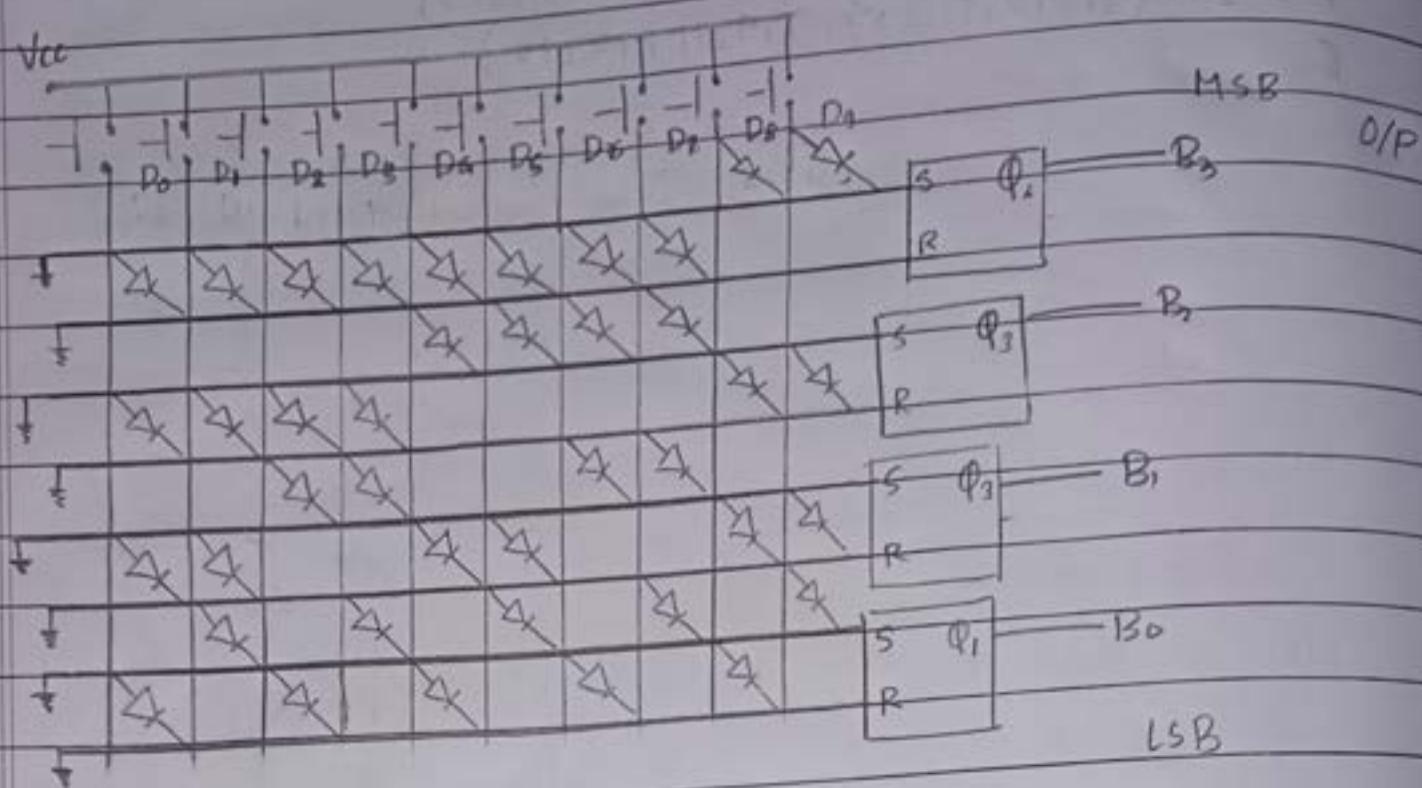

B₃ B₂ B₁ B₀

0 0 0 0

0 0 0 1

0 0 1 0

0 0 1 1

0 1 0 0

0 1 0 1


0 1 1 0

0 1 1 1

1 0 0 0

1 0 0 1

Decoder

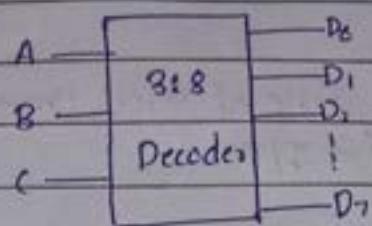

3 line to 8 line

T/P			O/P							
A	B	C	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = \bar{A}\bar{B}\bar{C}$$

$$D_1 = \bar{A}\bar{B}C$$

$$D_2 = \bar{A}BC$$


$$D_3 = \bar{A}B\bar{C}$$

$$D_4 = A\bar{B}\bar{C}$$

$$D_5 = A\bar{B}C$$


$$D_6 = AB\bar{C}$$

$$D_7 = ABC$$

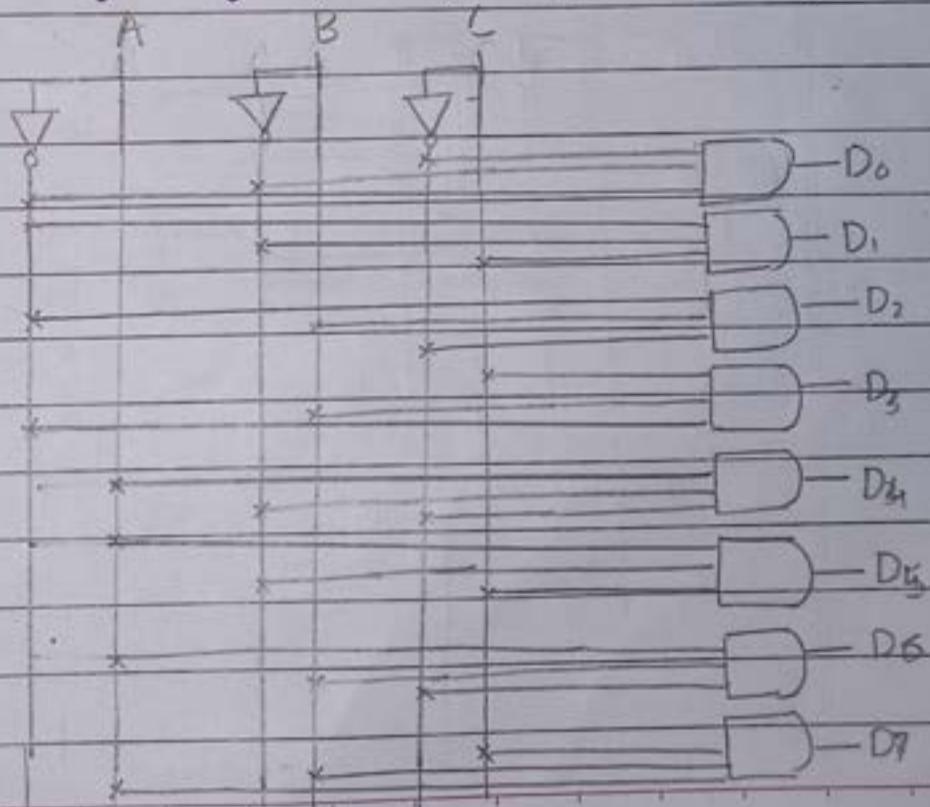

Multiplexers

Data

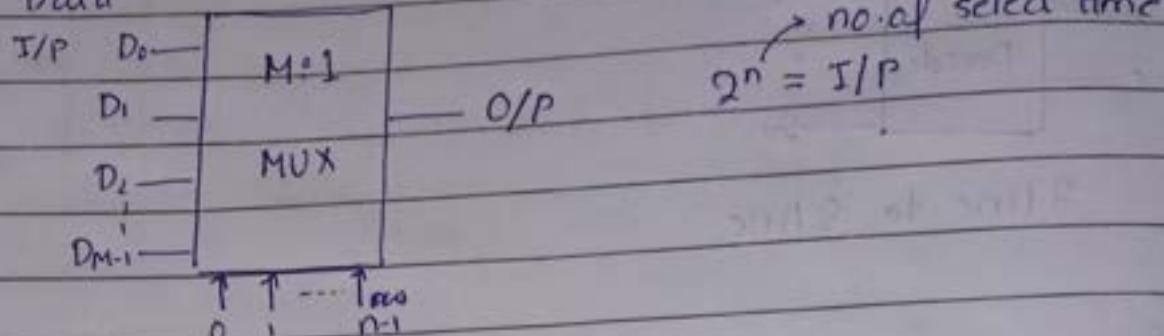


no. of select time

$$2^n = I/P$$

Select


I/P

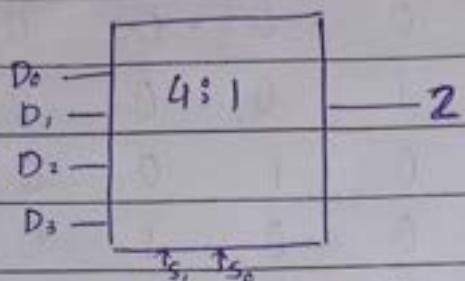


I/P	S_1, S_0	O/P
D_0	0 0	D_0
D_1	0 1	D_1
D_2	1 0	D_2
D_3	1 1	D_3

$$Z = D_0 \bar{S}_1 \bar{S}_0 + D_1 \bar{S}_1 S_0 + D_2 S_1 \bar{S}_0 + D_3 S_1 S_0$$


S_1, S_0

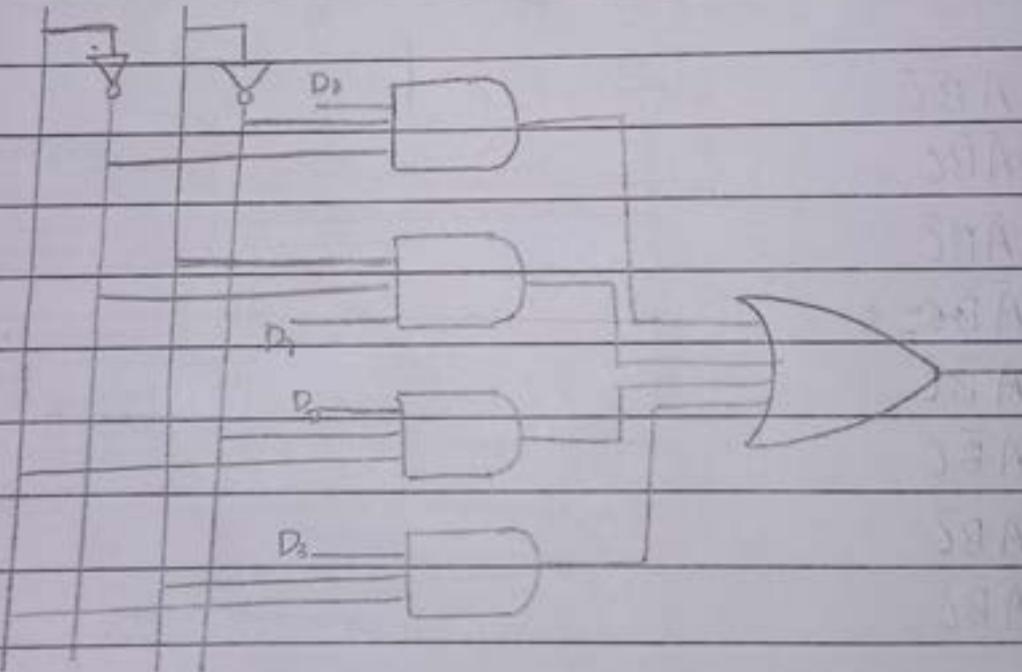


Q Design 4:1 MUX by using 2:1 MUX

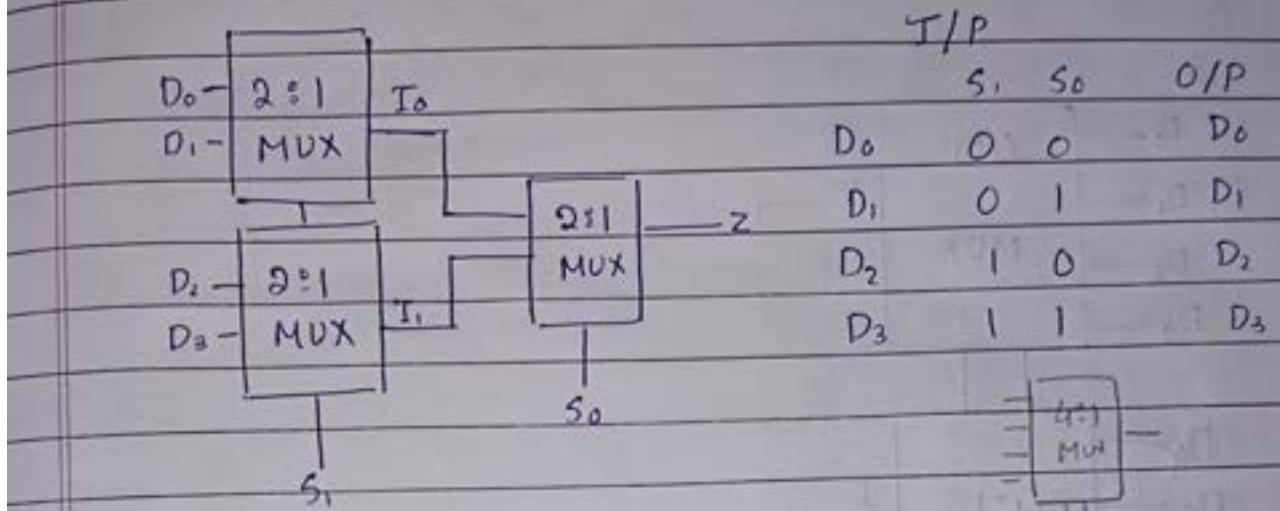

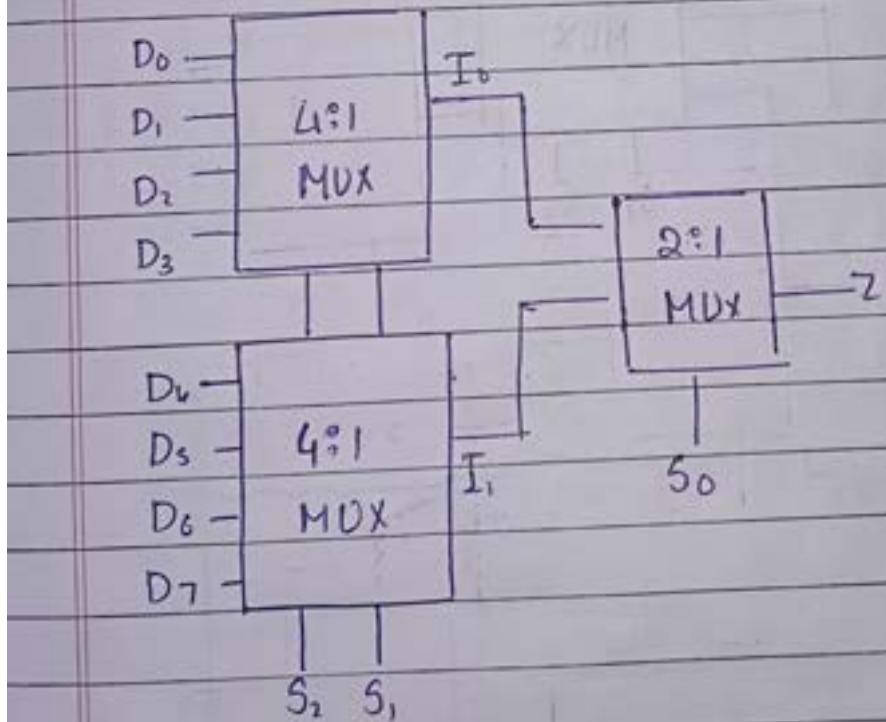
Q Draw a circuit for 8:1 MUX by using 4:1 MUX




→ Draw a circuit 16:1 MUX using 4:1 MUX

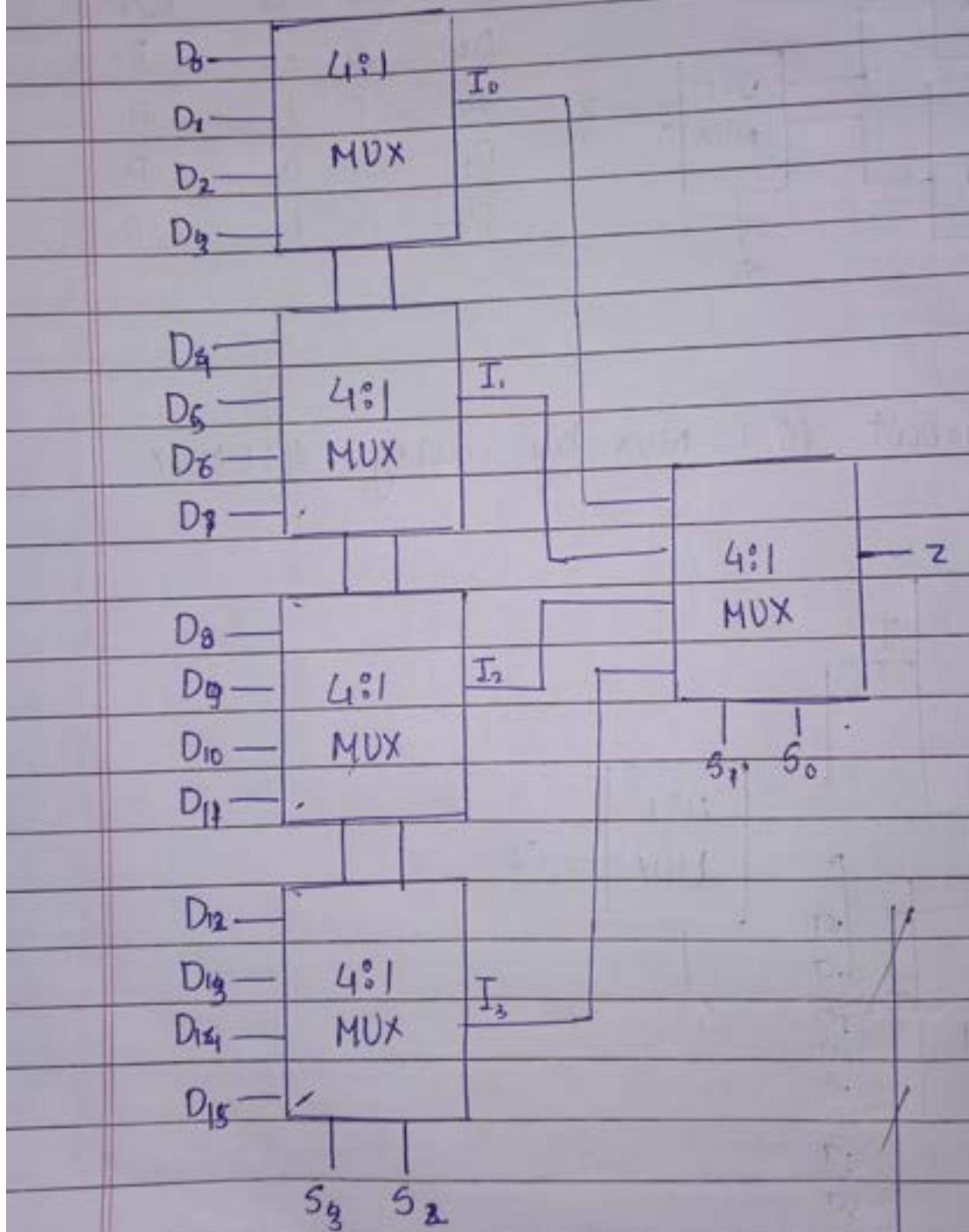

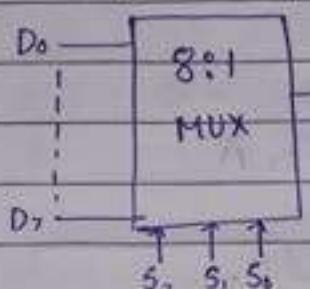→ Implement the function using one 8x1 MUX $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$



A	B	C	D
0	0	0	0
2	0	0	0
2	0	0	1
9	0	0	1
9	0	1	0
56	0	1	0
7	0	1	1
7	0	1	1
8	1	0	0
910	1	0	0
10	1	0	1
11	1	0	1
12	1	0	1
13	1	0	0
13	1	1	0
14	1	1	0
15	1	1	1

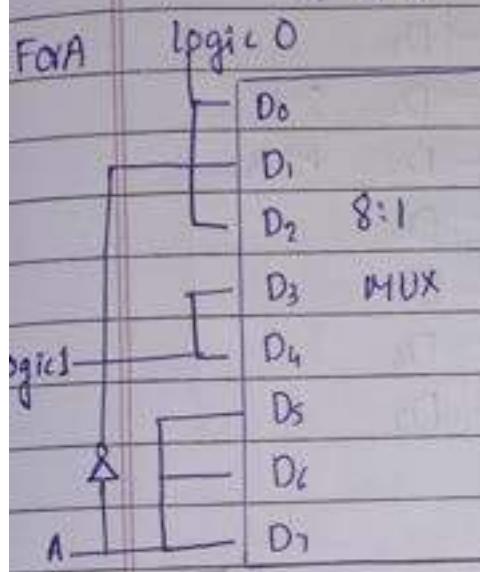

D0	D1	D2	D3	D4	D5	D6	D7	IS
Ā	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
0	Ā	0	1	1	A	A	A	




Q Implement the function using an 8x1 MUX
 $F(A, B, C, D) = \sum_m (0, 1, 2, 4, 5, 8, 10, 12, 13)$

	A	B	C	D
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0

For A


3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

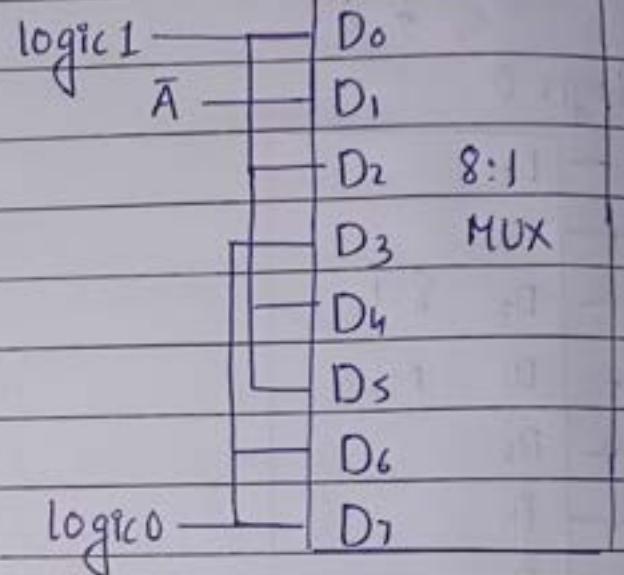

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	\bar{A}	1	0	1	1	0	0


For B

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{B}	0	1	2	3	8	9	10	11
B	4	5	6	7	12	13	14	15
I	1	1	\bar{B}	0	1	B	\bar{B}	0

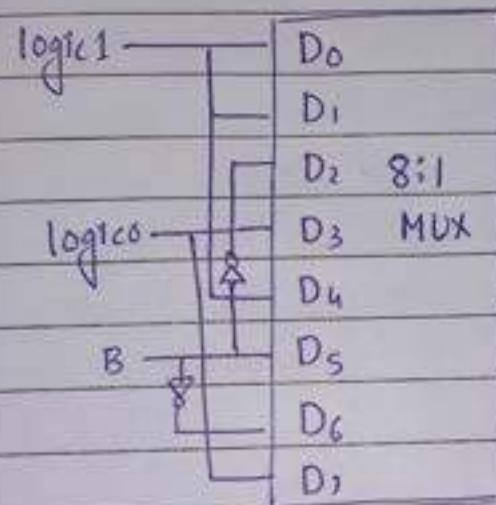


For C

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{B}	0	1	4	5	8	9	12	13
C	2	3	6	7	10	11	14	15
I	1	\bar{C}	\bar{C}	\bar{C}	1	0	\bar{C}	\bar{C}

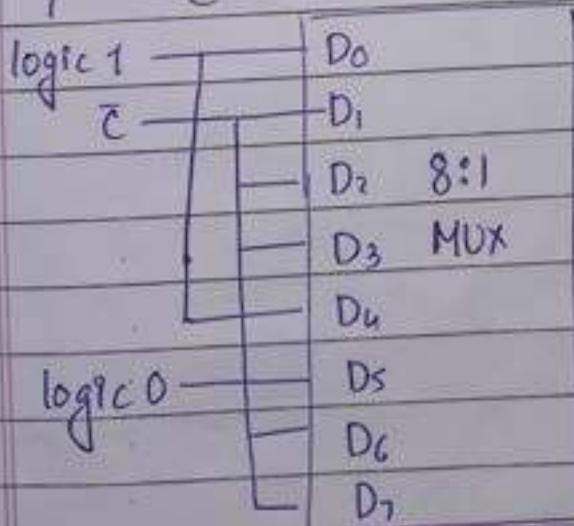

For D

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
D	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
	1	\bar{D}	1	0	\bar{D}	\bar{D}	1	0

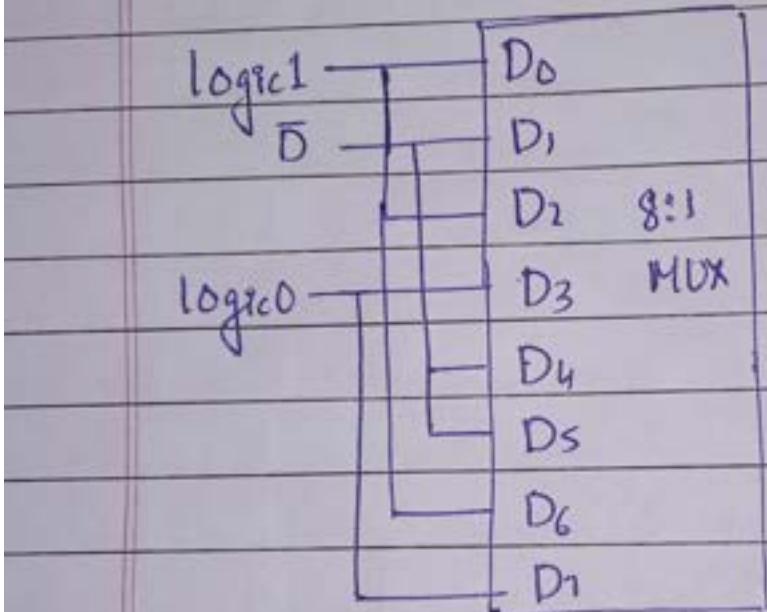

Unit : 4

Page No. _____



Sequential logic & Sequential Circuit

Date _____


Combinational Ckt


Sequential Ckt

- | | |
|--|---|
| 1] Output is depend on present I/P | 1] Output is depend on present I/P and past output. |
| 2] Memory element is absent | 2] Memory element is present |
| 3] Basic building blocks are all basic logic gates. | 3] Basic building blocks are Flip Flop |
| 4] Easy to design | 4] Complex to design |
| 5] No clock signal is applied. | 5] Clock signal is required. |
| 6] Ex: Half & Full adder, encoder, decoder, MUX, DeMUX | 6] Ex: Flip Flop, counter, register |

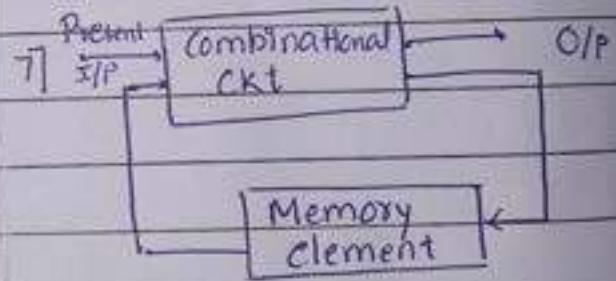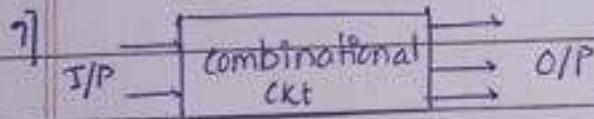

Latch

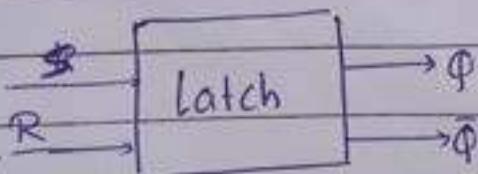

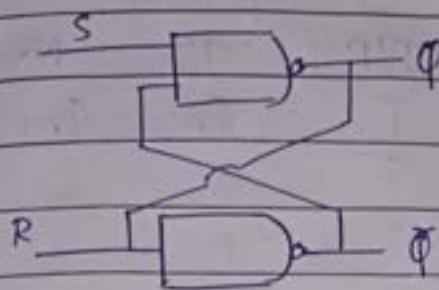

S	R	Q_n	Q_{n+1}
0	0	0	x ? } invalid state
0	0	1	x } state
0	1	0	1 ? set
0	1	1	1 }
1	0	0	0 ? reset
1	0	1	0 }
1	1	0	0 ? NC
1	1	1	1 }

Truth Table SRFF

I/P	PS	NS
S R	Q_n	Q_{n+1}
0 0	0	0 ?
0 0	1	1 } NC
0 1	0	0 ?
0 1	1	0 } Reset

1 0 0 1 ? set

1 0 1 1 }

1 1 0 x ? invalid

1 1 1 x }





D - Flip Flop

I/P	PS	NS
D	Q_n	Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

D Q_{n+1}

0 0

1 1

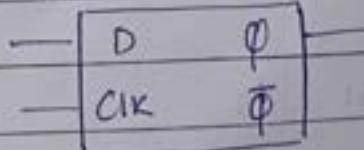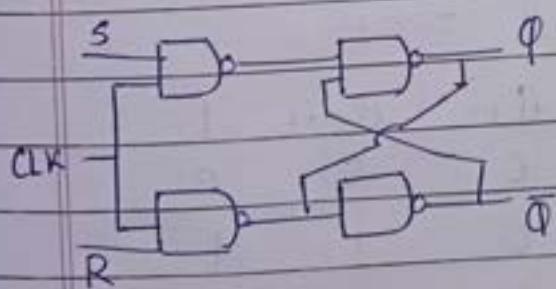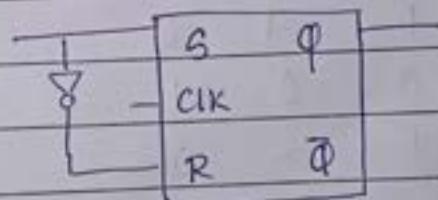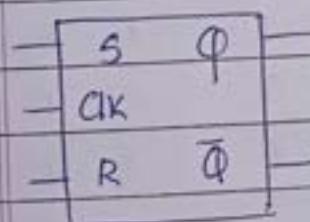

J-K Flip Flop

I/P PS NS

J K Q_n Q_{n+1}

0 0 0 0 } NC

0 0 1 1 } NC

0 1 0 0 } Reset

0 1 1 0 } NC

1 0 0 1 } Set

1 0 1 1 } Invalid

1 1 0 1 } Invalid

1 1 1 0 }

T-Flip Flop

I/P PS NS



T Q_n Q_{n+1}

0 0 0 } 0

0 1 1 } 1 } NC

1 0 1 } 0 } NC

1 1 1 } 0 } T

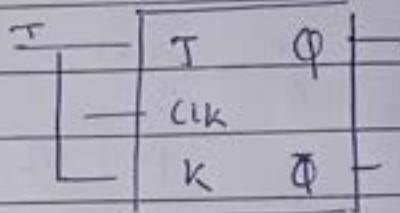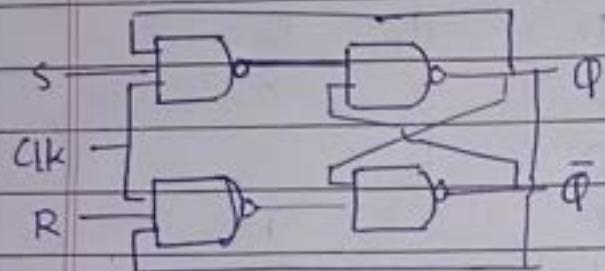Excitation1] S-R FF Q_n Q_{n+1} S R

0 0 0 x

0 1 1 0

1 0 0 1

1 1 x 0

2] J-K FF Q_n Q_{n+1} J K

0 0 0 x

0 1 1 x

1 0 x 1

1 1 x 0

3] D FF Q_n Q_{n+1} D

0 0 0

0 1 1

1 0 0

4] T FF Q_n Q_{n+1} T


0 0 0

0 1 1

1 0 1

Conversion of Flip Flop

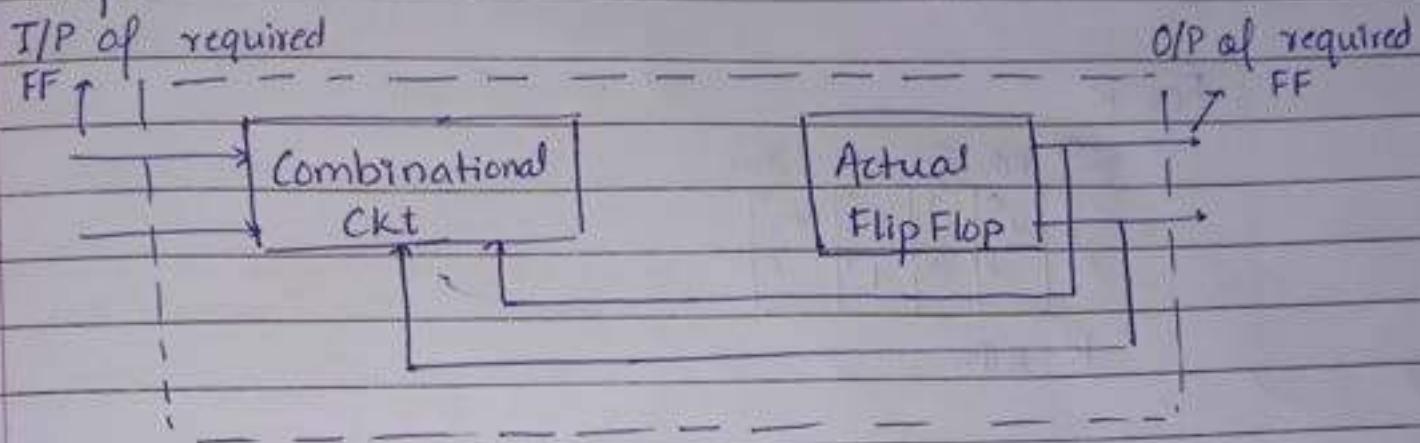To convert one type of flip flop into another type we have to obtain the expression for inputs of the existing flip flop in terms of the input of the required flip flop and the present state variables of the existing and implement them.



Convert SRFF to JKFF

1. Conversion Table

External I/P		Present state Q_n	Next state Q_{n+1}	Flip Flop I/P	
J	K			S	R
0	0	0	0	0	x
0	0	1	1	x	0
0	1	0	0	0	x
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	x	0
1	1	0	1	1	x
1	1	1	0	x	1

2. Kmap For S-R

For S

	KQ_n	$\bar{K}Q_n$	$\bar{K}\bar{Q}_n$	$K\bar{Q}_n$	$K\bar{\bar{Q}}_n$
\bar{J}	0	X	1	3	?
J	1	X ^s		1	1


$$S = J\bar{Q}_n$$

For R

	KQ_n	$\bar{K}Q_n$	$\bar{K}\bar{Q}_n$	$K\bar{Q}_n$	$K\bar{\bar{Q}}_n$
\bar{J}	X	0	1	3	X
J	4	S	1	7	6

$$R = K\bar{Q}_n$$

3] logic diagram

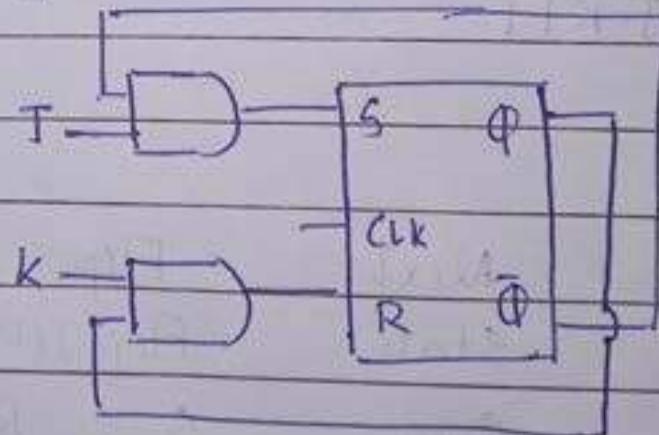

→ Convert DFF to SRFF

External
I/P

Present
state

Next
state

D SR

Q

Q-bar

~~A.W~~

Convert JK to SR

Convert SR to D

Convert JK to D

Convert D to JK


Unit 5 :

Finite State Machine


1] Mealy state Machine

2] Moore state Machine


Mealy state Machine

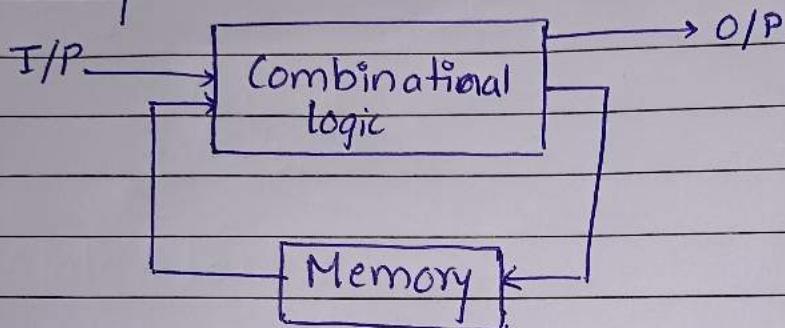


Moore state Machine

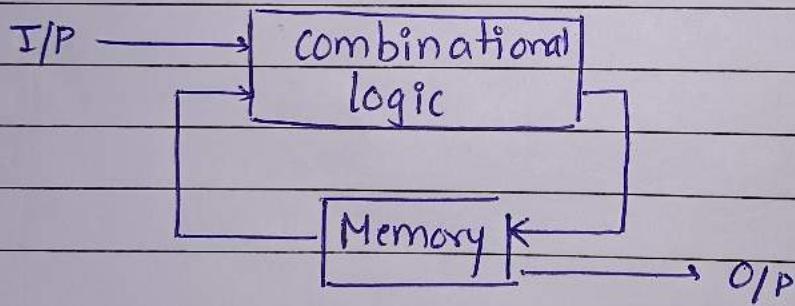


① Mealy state machine

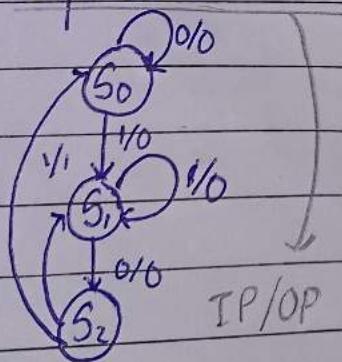

② Moore state machine

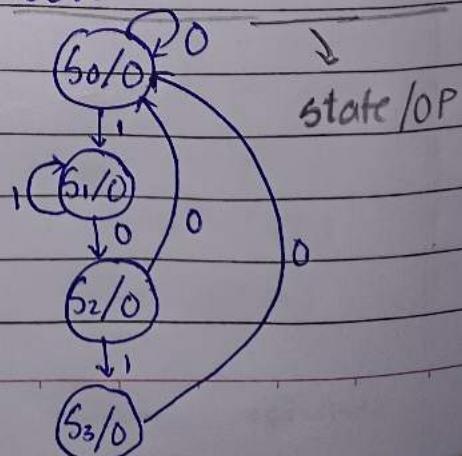

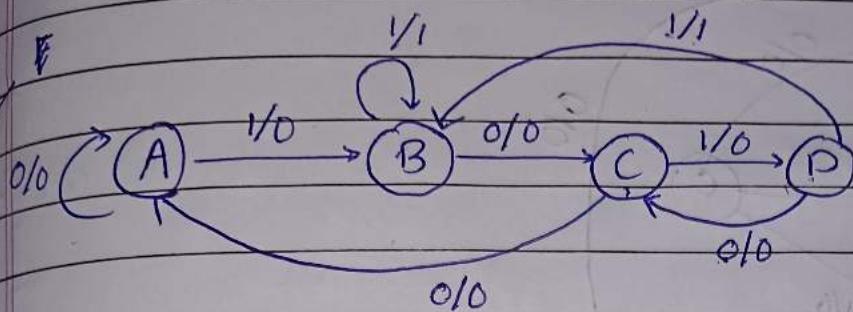



State Table

Present state	Nearest state		O/P Z	
	$n=0$	$n=1$	$n=0$	$n=1$
A	A	B	0	0
B	$C = A$	B	0	1
C	A	$D = B$	0	0
P	C	B	0	1

Reduced state table

PS	NS		O/P	
	$n=0$	$n=1$	$n=0$	$n=1$
A	A	B	0	0
B	A	B	0	1

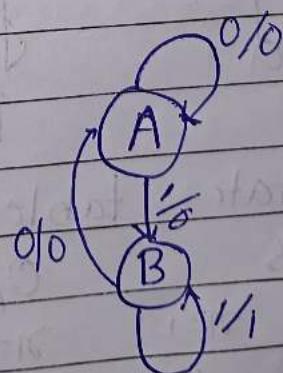

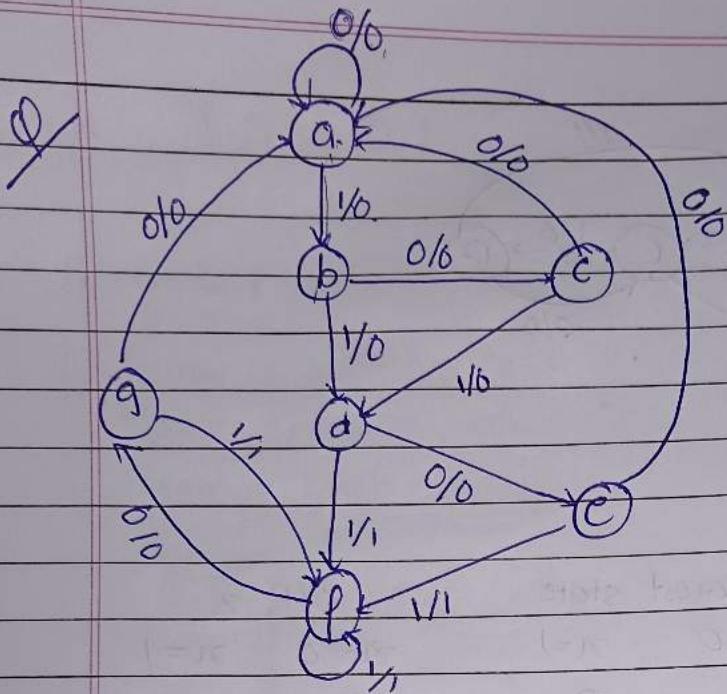

State table

	$n=0$	$n=1$	$n=0$	$n=1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	c	f=d	0	1
e	a	f=d	0	1
f	g=e	f	0	1
g=e	x	a	0	1
g	x	f		



Reduced state table

PS NS O/P

 $n=0 \quad n=1 \quad n=0 \quad n=1$

a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	c	d	0	1
e	a	d	0	1


Date / /

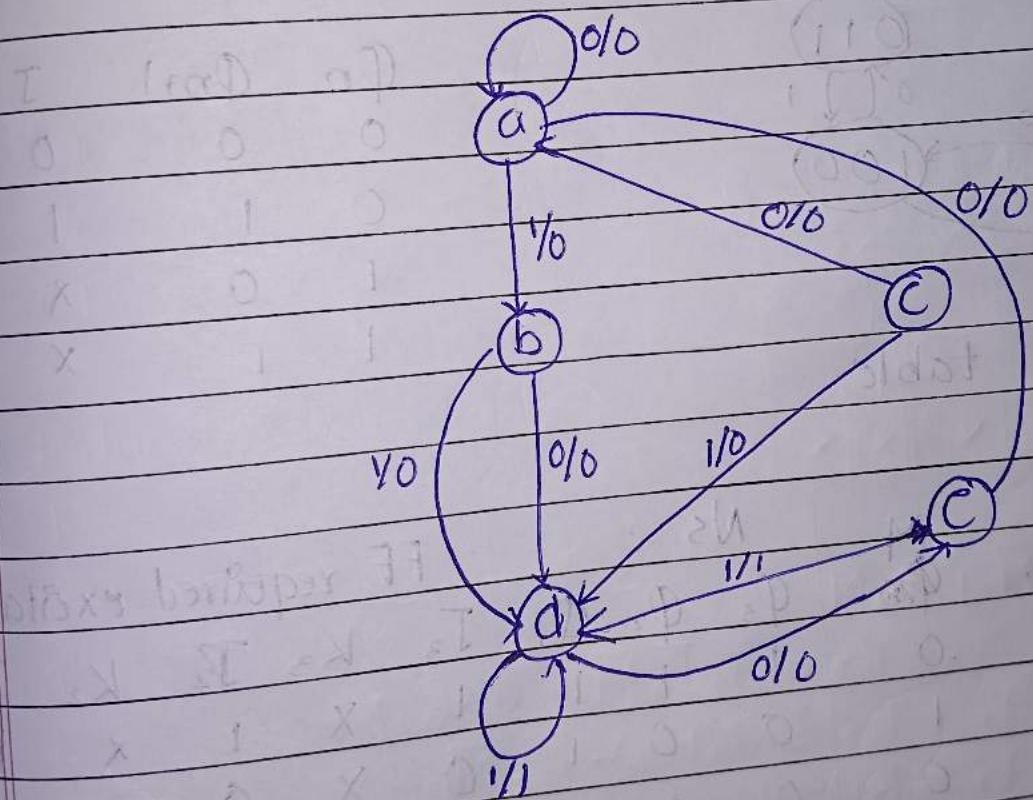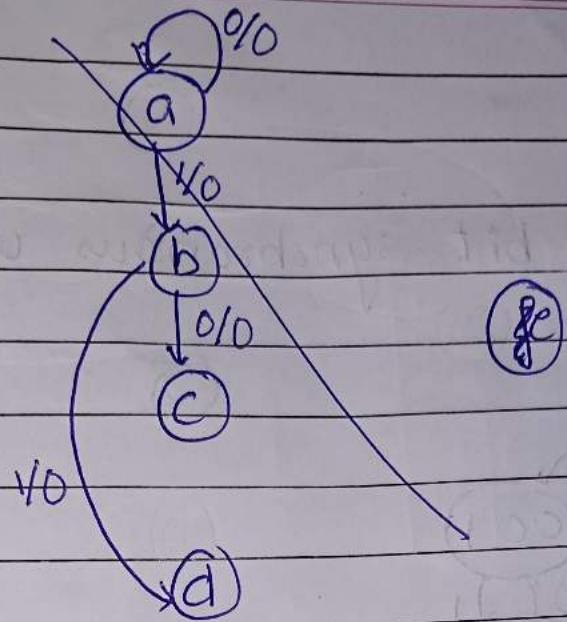

Counter

Q. Design a 3-bit synchronous up-down counter.

i] State dia

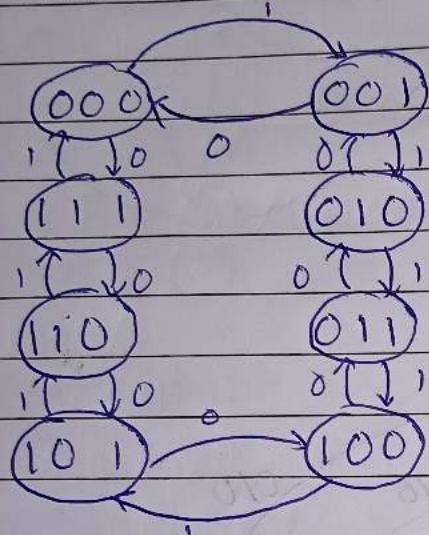

Φ_n	Φ_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

2] Excitation table

PS				Ns			FF required excitation type					
Φ_3	Φ_2	Φ_1	M	Φ_3	Φ_2	Φ_1	J_3	K_3	J_2	K_2	J, K,	
0	0	0	0	1	1	1	1	x	1	x	1	x
0	0	0	1	0	0	1	0	x	0	x	1	x
0	0	1	0	0	0	0	0	x	0	x	x	1
0	0	1	1	0	1	0	0	x	1	x	x	1
0	1	0	0	0	0	1	0	x	x	1	1	x
0	1	0	1	0	1	1	0	x	x	0	1	x
0	1	1	0	0	1	0	0	x	x	0	x	1
0	1	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	1	1	x	1	1	x	1	x
1	0	0	1	1	0	1	x	0	0	x	1	x

Φ_3	Φ_2	Φ_1	M	$\bar{\Phi}_3$	$\bar{\Phi}_2$	$\bar{\Phi}_1$	J_3	K_3	J_2	K_2	J_1	K_1
1	0	1	0	1	0	0	X	0	0	X	0	1
1	0	1	1	1	1	0	X	0	1	X	1	1
1	1	0	0	1	0	1	X	0	1	1	1	X
1	1	0	1	1	1	1	X	0	0	1	X	1
1	1	1	0	1	1	0	X	0	0	0	X	1
1	1	1	1	0	0	0	X	1	1	X	1	1

→ For J_3

$\Phi_3\bar{\Phi}_2/\bar{\Phi}_1M$	$\bar{\Phi}_1\bar{M}$	$\bar{\Phi}_1M$	Φ_1M	$\Phi_1\bar{M}$
$\Phi_3\bar{\Phi}_2$	1 0	1	3	2
$\bar{\Phi}_3\Phi_2$	4	5	1 7	6
$\Phi_3\Phi_2$	X^{12}	X^{13}	X^{15}	X^{16}
$\bar{\Phi}_3\bar{\Phi}_2$	X^8	X^9	X^{11}	X^{10}

$$J_3 = \bar{\Phi}_2 \bar{\Phi}_1 \bar{M} + \Phi_2 \Phi_1 M$$

→ For K_3

$\Phi_3\bar{\Phi}_2/\bar{\Phi}_1M$	$\bar{\Phi}_1\bar{M}$	$\bar{\Phi}_1M$	Φ_1M	$\Phi_1\bar{M}$
$\Phi_3\bar{\Phi}_2$	1 0	X^1	X^3	X^2
$\bar{\Phi}_3\Phi_2$	X^4	X^5	X^7	X^6
$\bar{\Phi}_3\Phi_2$	X^{12}	X^{13}	1 15	14
$\Phi_3\bar{\Phi}_2$	1 8	9	11	10

$$K_3 = \bar{\Phi}_2 \bar{\Phi}_1 \bar{M} + \Phi_2 \Phi_1 M$$

→ For J_2

$\Phi_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	X^4	X^5	X^7	X^6					
$\bar{\Phi}_3 \Phi_2$	X^{12}	X^{13}	X^{15}	X^{14}					
$\Phi_3 \Phi_2$	X^1	X^3	X^2						
$\Phi_3 \bar{\Phi}_1$	1^8	1^9	1^{10}	1^{11}					

$$J_2 = \bar{\Phi}_3 \bar{\Phi}_2 + \bar{\Phi}_3 \Phi_2 + \Phi_3 \Phi_2 + \bar{\Phi}_3 \bar{\Phi}_1 + \bar{\Phi}_3 \Phi_1 + \Phi_3 \Phi_1$$

→ For K_2

$\Phi_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	X^4	X^5	X^7	X^6					
$\bar{\Phi}_3 \Phi_2$	1^8	1^9	1^{10}	1^{11}					
$\Phi_3 \Phi_2$	X^1	X^3	X^2						
$\Phi_3 \bar{\Phi}_1$	X^0	X^1	X^3	X^2					

$$K_2 = \bar{\Phi}_3 \bar{\Phi}_2 + \Phi_3 \Phi_2$$

→ For T_{B1}


$\Phi_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \bar{\Phi}_2$	$\bar{\Phi}_3 \Phi_2$	$\Phi_3 \Phi_2$	$\Phi_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \bar{\Phi}_1$	$\bar{\Phi}_3 \Phi_1$	$\Phi_3 \Phi_1$	$\Phi_3 \bar{\Phi}_0$	$\bar{\Phi}_3 \bar{\Phi}_0$
$\bar{\Phi}_3 \bar{\Phi}_2$	X^4	X^5	X^7	X^6					
$\bar{\Phi}_3 \Phi_2$	1^8	1^9	X^{10}	X^{11}					
$\Phi_3 \Phi_2$	X^1	X^3	X^2						
$\Phi_3 \bar{\Phi}_1$	1^0	1^1	X^3	X^2					

$$T_{B1} = 1$$


→ For K_1

$\bar{Q}_3 Q_1$	$\bar{Q}_2 \bar{Q}_1 M$	$\bar{Q}_2 M$	$Q_3 M$	$Q_3 \bar{M}$
$\bar{Q}_3 Q_1$	X ⁰	X ¹	I ³	I ²
$\bar{Q}_3 Q_1$	X ⁴	X ⁵	I ⁷	I ⁶
$\bar{Q}_3 Q_1$	X ¹²	X ¹³	I ¹⁵	I ¹⁴
$\bar{Q}_3 Q_1$	X ⁸	X ⁹	I ¹⁰	I ¹¹

$$K_1 = 1$$

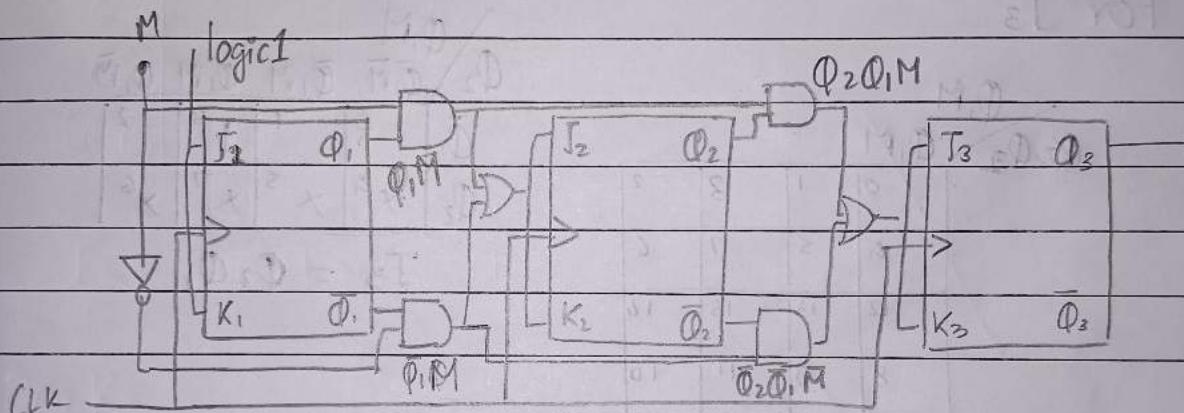

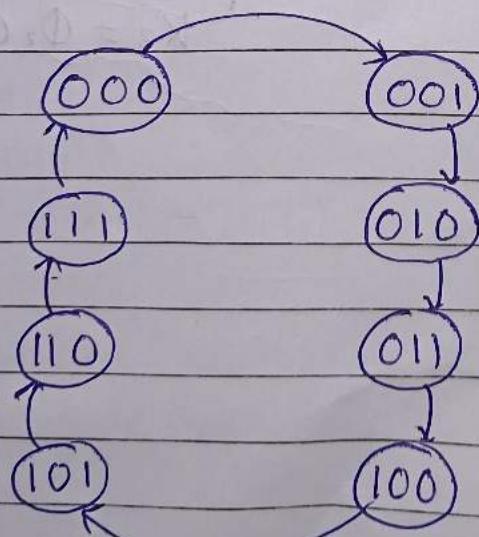3-bit synchronous up counter by using JK FF



$$J_3 = K_3 = \Phi_2 \oplus 1,$$

$$J_2 = K_2 = \Phi,$$


$$J_1 = K_1 = 1$$

Page No. _____

Date _____ / _____ / _____

PS						NS		FF required			
Φ_3	Φ_2	Φ_1	Φ_3	Φ_2	Φ_1	J_3	K_3	J_2	K_2	J_1	K_1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	X	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

logic1

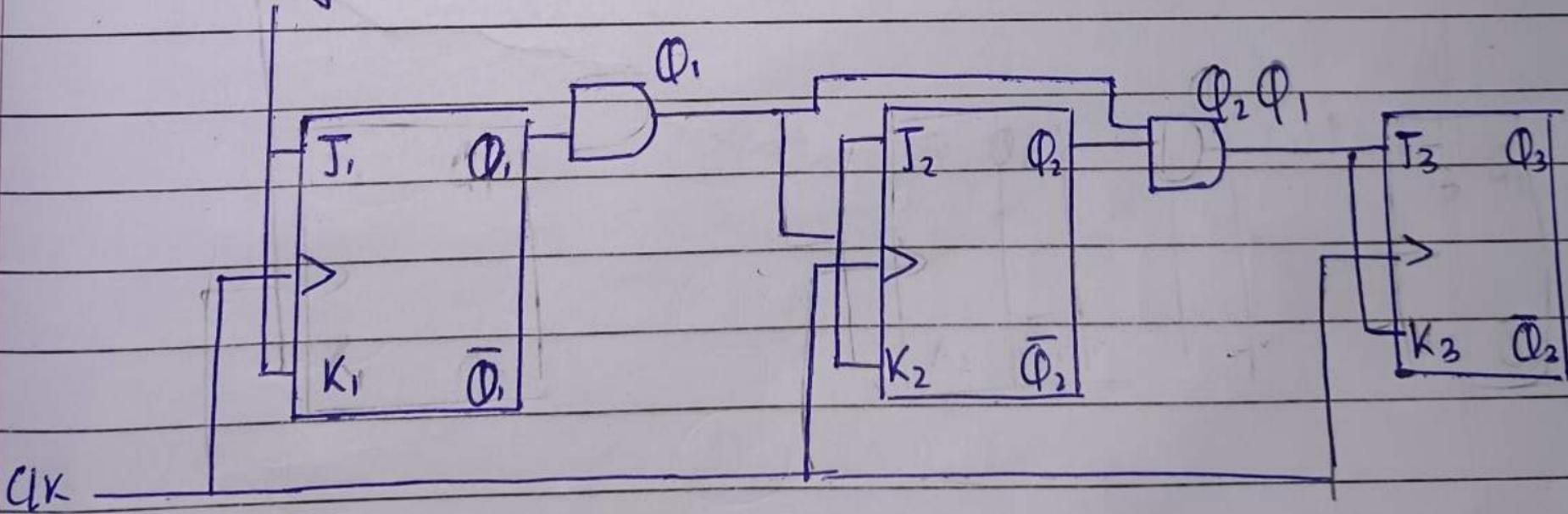

Serial in 11th out → SIPO
11th in serial out → PISO
11th in 11th out → PIPO

Page No. _____

Date ____ / ____


Registers:

Q How many ways can be transfer data in register?


Ans:

#


1] SISO

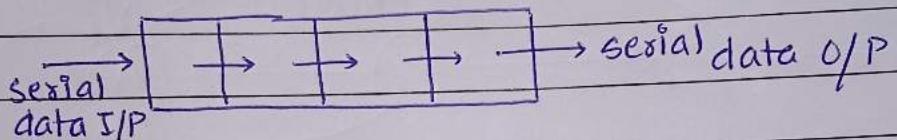


2] SIPO

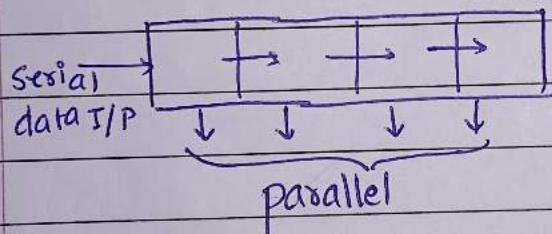


3] PISO Parallel data input

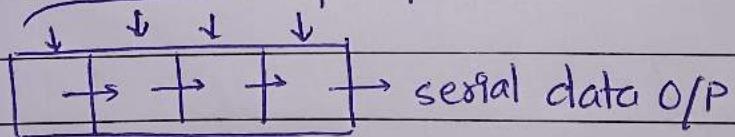

4] PIPO Parallel data I/P

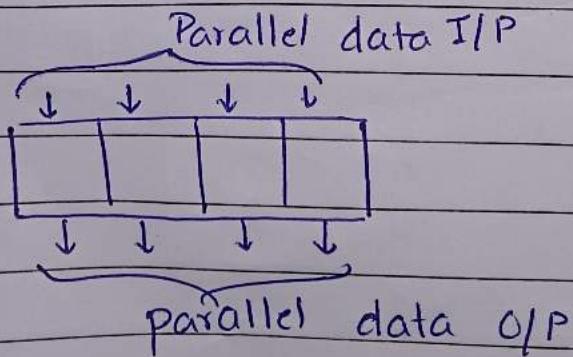


5]

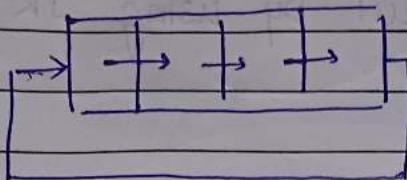



Rotate right shift

6]


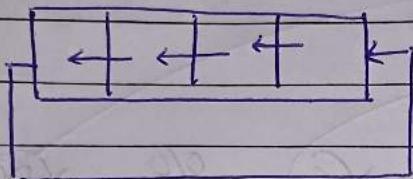


Rotate left shift

SISO

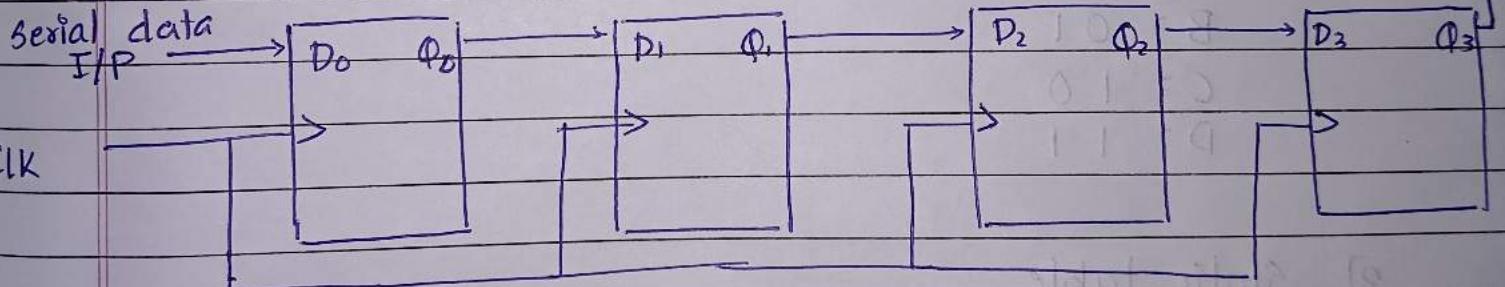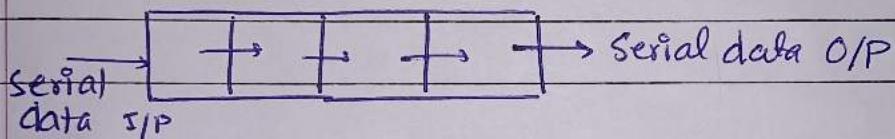

CLK	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	1	0	0
4	1	0	0	0
5	0	0	0	0

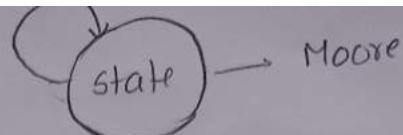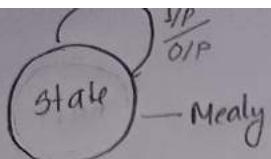


Page No. _____
Date / /

Q) Implement mealy circuit by using JK FF for sequence 0101

- ① State diagram
- ② Code assignment
- ③ State Table
- ④ Minimal expression using K-map
- ⑤ Circuit diagram

→ 1] Non-overlapping

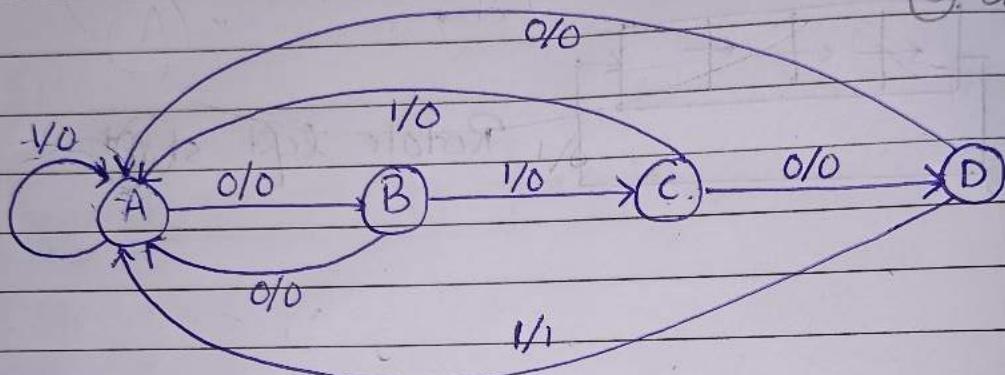

2] Code assignment

$$A = 00$$

$$B = 01$$

$$C = 10$$

$$D = 11$$

3] Static table

Present state	Next state		O/P	
	$n=0$	$n=1$	$n=0$	$n=1$
A	B	A	0	0
B	A	C	0	0
C	D	A	0	0
D	A	A	0	1


P.S.

N.S


 Φ_{10} $n=0 \quad n=1$

$\Phi_1 \Phi_0$	$\Phi_1 \Phi_0$	$\Phi_1 \Phi_0$	$J_1 \quad K_1 \quad J_0 \quad K_0$	J_1, K_1, J_0, K_0
0 0	0 1	0 0	0 X	1 X
0 1	0 0	1 0	0 X	X 1
1 0	1 1	0 0	X 0	1 X
1 1	0 0	0 0	X 1	X 1

excitation required

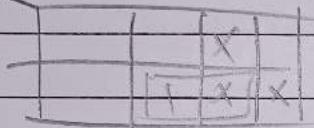 $n=0 \quad n=1$ For J_1 ~~$\Phi_1 \Phi_0$~~ n 

$$J_1 = n \cdot \Phi_0$$

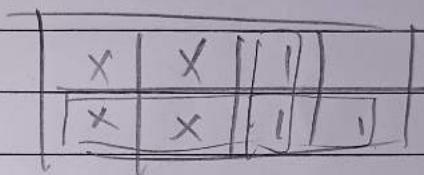For K_1 

$$K_1 = n + \Phi_1 \Phi_0$$